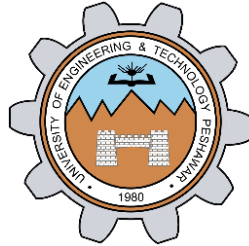


LAB # 6



CSE-203L Circuit & Systems-II Lab

Fall 2022

Submitted by: Ali Asghar

Registration No.: 21PWCSE2059

Class Section: C

“On my honor, as student of University of Engineering and Technology, I have neither given nor received unauthorized assistance on this academic work.”

Student Signature: _____

Submitted to:

Engr. Faiz Ullah

29th November, 2022

Department of Computer Systems Engineering
University of Engineering and Technology, Peshawar

TITLE:

AC Superposition

OBJECTIVES:

- To Analyze multi-source AC Circuits using AC Superposition Theorem.
- To study

APPARATUS:

- Oscilloscope
- AC Function Generator

COMPONENTS:

- 0.1 μ F Capacitor
- 10 mH Inductor
- 1k Ω Resistor

THEORY OVERVIEW:

The Superposition Theorem can be used to analyze multi-source AC linear bilateral networks. Each source is considered in turn, with the remaining sources replaced by their internal impedance, and appropriate series-parallel analysis techniques employed. The resulting signals are then summed to produce the combined output signal. To see this process more clearly, the exercise will utilize two sources operating at different frequencies. Note that as each source has a different frequency, the inductor and capacitor appear as different reactance to the two sources.

SUPERPOSITION PRINCIPLE:

The principle of superposition says that the output of a linear circuit due to several inputs working together is equal to the sum of the outputs working separately. The inputs to the circuit are the voltages of the independent voltage sources and the currents of the independent current sources.

CIRCUIT DIAGRAM:

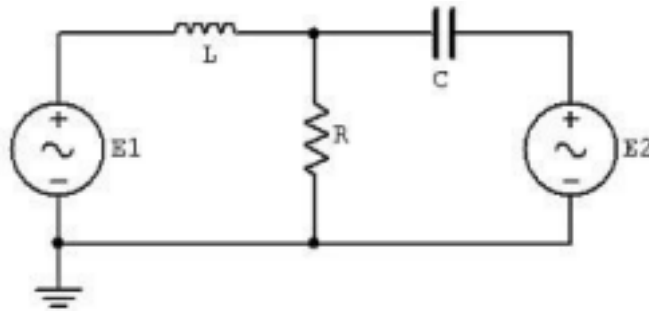


Figure 1

PROCEDURE:

To test the Superposition Theorem, sources E1 and E2 will be examined separately and then together.

SOURCE ONE ONLY

1. Consider the circuit of Figure 1 with $C=0.1\ \mu\text{F}$, $L=10\text{mH}$, $R=1\text{k}\Omega$, using only source $E1=2\text{ V p-p}$ at 1 kHz and with source $E2$ replaced by a 0-V voltage source represented as a short circuit. Using standard series parallel techniques; calculate the voltages across R . Record the results in Table 1.
2. Build the circuit of Figure 1 using $C=0.1\ \mu\text{F}$, $L=10\text{mH}$, and $R=1\text{k}\Omega$. Replace $E2$ with 0-V voltage source represented as a short circuit. Set $E1$ to 2V p-p at 1 kHz , unloaded. Place probe one across $E1$ and probe two across R . Measure the voltages across R , and record in Table 1.

SOURCE TWO ONLY

1. Consider the circuit of Figure 1 using only source $E2=2\text{ V p-p}$ at 10 kHz and with source $E1$ replaced by 0-V voltage source represented as a short circuit. Using standard series-parallel techniques; calculate the voltages across R . Record the results in Table 2.
2. Replace the short circuit with source $E2$ and set it to 2Vp-p at 10 kHz , unloaded. Replace $E1$ with 0-V voltage source represented as a short circuit. Place probe one across $E2$ and probe two across R . Measure the voltages across R and record in Table 2.


SOURCES ONE AND TWO

1. Consider the circuit of Figure 1 using both sources, $E_1=2V_{p-p}$ at 1 kHz and $E_2=2V_{p-p}$ at 10 kHz. Add the calculated voltages across R from Tables 1 and 2. Record the results in Table 3. 6. Replace the short circuit with source E1 and set it to $2V_{p-p}$ at 1 kHz, unloaded. Both sources should now be active. Place probe one across R. Measure the voltages across R, and record in Table 3.
2. Repeat the experiment for 1 μ F capacitor, 1mH inductor and 1k Ω resistor.

OBSERVATIONS:

- a) For $V(p-p) = 2V$, $f_1 = 1KHz$, $f_2 = 10KHz$, $R = 1k\Omega$, $L = 10mH$, and $C = 0.1\mu F$

CIRCUIT DESIGN IN PROTEUS:

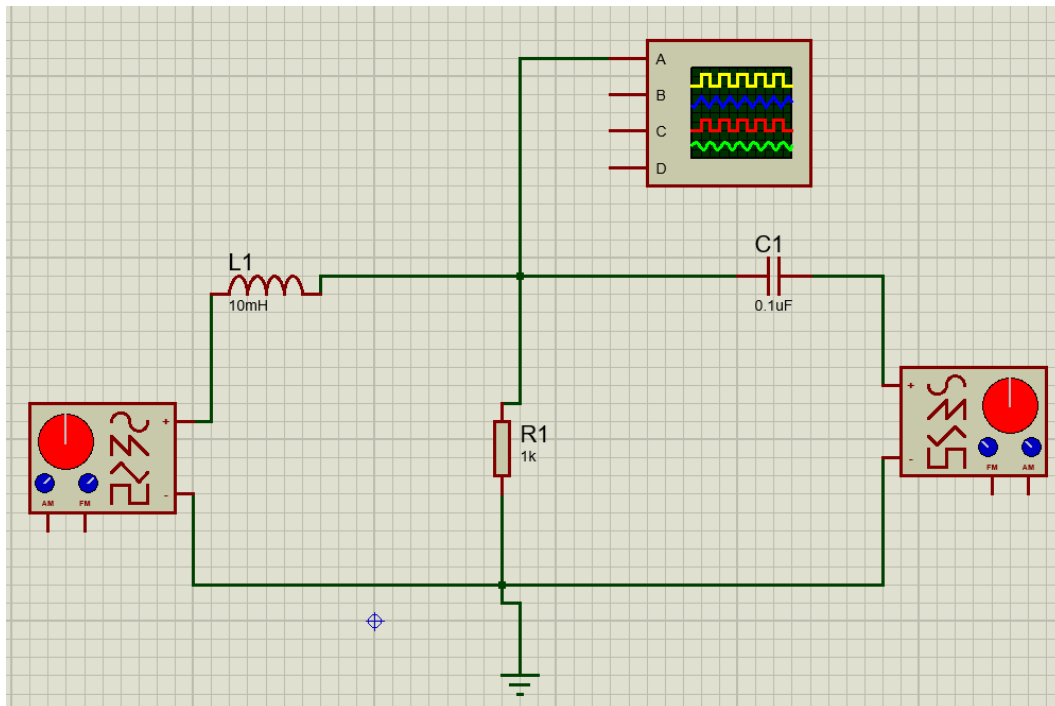


MATLAB CODE:

```
Editor - D:\MatlabWork\lab6.m
lab6.m x +
1 -   clc
2 -   clear all
3
4 -   a1 = -1591550j/(1000 - 1591.55j);
5 -   b1 = 62.83j + a1;
6 -   Vr1 = a1/b1 * (2+0j);
7
8 -   M1 = abs(Vr1);
9 -   theta1 = angle(Vr1);
10 -  deg1 = theta1 * (180/pi);
11
12 -  a2 = 628320j/(1000 + 628.32j);
13 -  b2 = -159.15j + a2;
14 -  Vr2 = a2/b2 * (2+0j);
15
16 -  M2 = abs(Vr2);
17 -  theta2 = angle(Vr2);
18 -  deg2 = theta2 * (180/pi);
19
20 -  t = 0:0.000001:0.003;
21 -  f1 = 1000;
22 -  f2 = 10000;
23 -  w1 = 2*pi*f1;
```

```
Editor - D:\MatlabWork\lab6.m
lab6.m x +
20 -  t = 0:0.000001:0.003;
21 -  f1 = 1000;
22 -  f2 = 10000;
23 -  w1 = 2*pi*f1;
24 -  w2 = 2*pi*f2;
25 -  Vr1 = M1*sin(w1*t + deg1);
26 -  Vr2 = M2*sin(w2*t - deg2);
27 -  Vr = Vr1 + Vr2;
28
29 -  subplot(311)
30 -  plot(t,Vr1)
31 -  grid on
32 -  title('Source one only')
33
34 -  subplot(312)
35 -  plot(t,Vr2)
36 -  grid on
37 -  title('Source two only')
38
39 -  subplot(313)
40 -  plot(t,Vr)
41 -  grid on
42 -  title('Both Sources')
```

CODE OUTPUT:

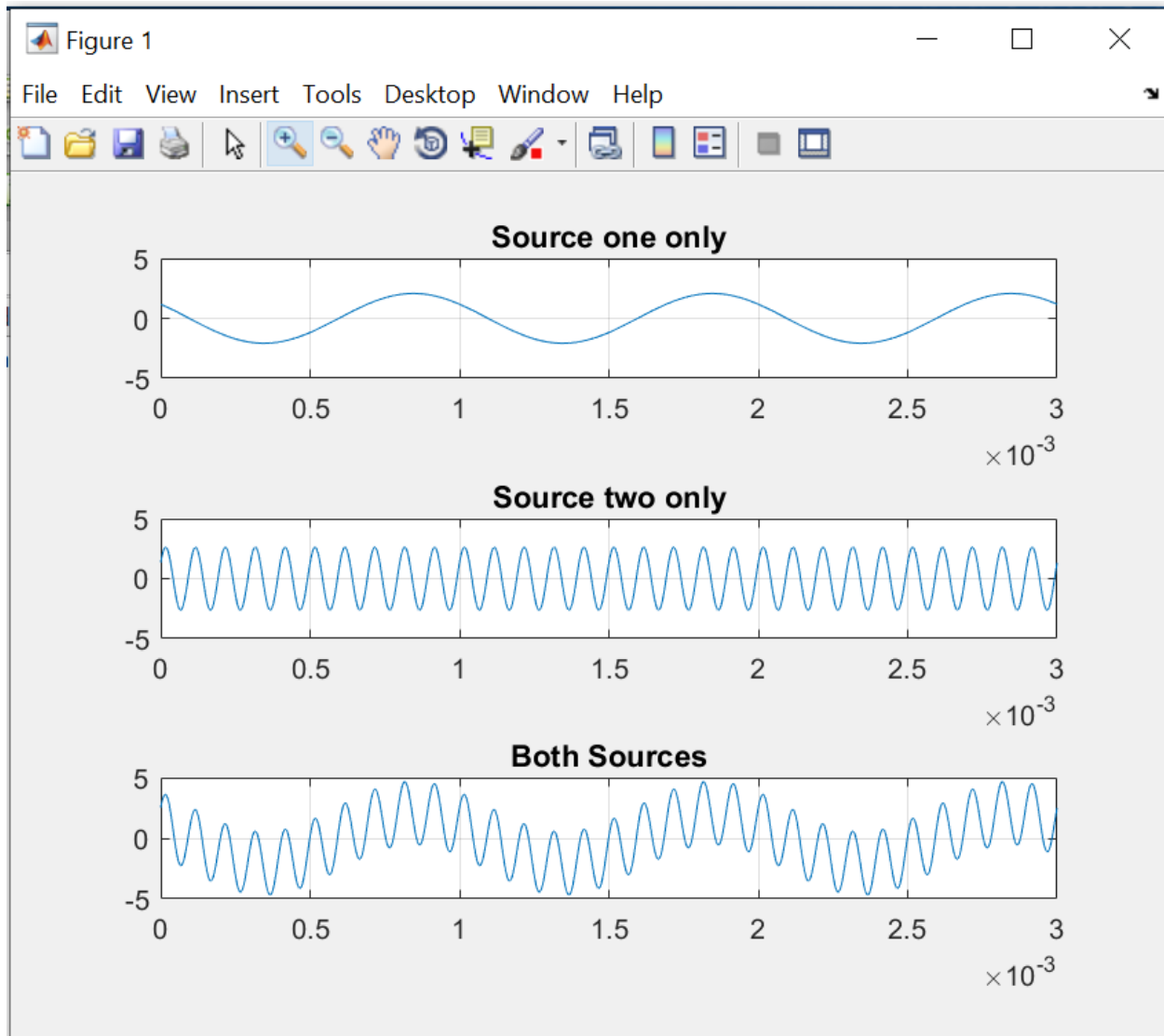

SOURCE 1 ONLY:

Table 1

	Theoretical	Experimental	%Deviation
V_R	2 V	2.1 V	%

SOURCE 2 ONLY:

Table 2

	Theoretical	Experimental	%Deviation
V_R	2.7 V	2.5 V	%


SOURCES 1 AND 2:

Table 3

	Theoretical	Experimental	%Deviation
V_R	4.6 V	4.56 V	%

b) For $V(p-p) = 2V$, $f_1 = 1KHz$, $f_2 = 10KHz$, $R = 1k\Omega$, $L = 10mH$, and $C = 1\mu F$

CIRCUIT DESIGN IN PROTEUS:

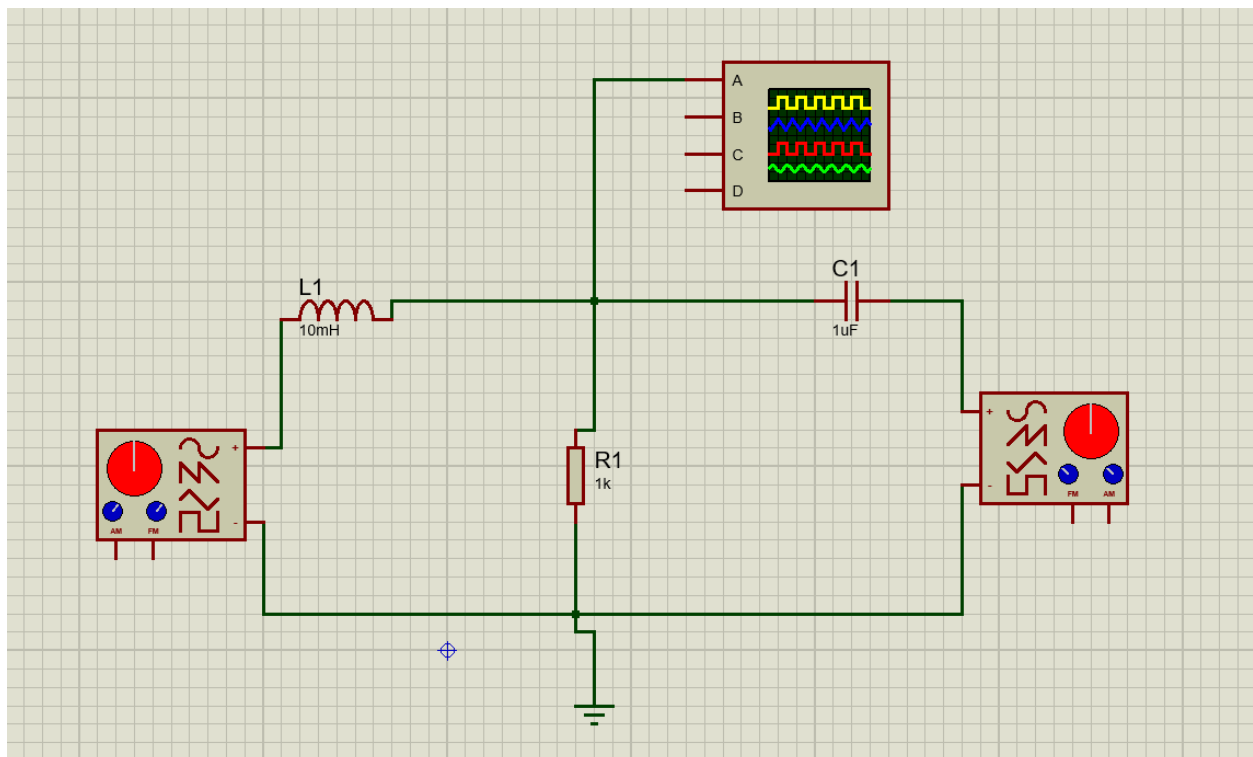


MATLAB CODE:

```
Editor - D:\MatlabWork\lab6For1uF.m
lab6For1uF.m x +
1 -   clc
2 -   clear all
3
4 -   R = 1000;
5 -   Zc1 = -1591.5i;
6 -   Ze1 = (R*Zc1)/(R + Zc1);
7 -   Zl1 = 2*pi*1000*0.01i;
8 -   Vr1 = (Ze1)/(Zl1 + Ze1) * (2+0j);
9
10 -  M1 = abs(Vr1);
11 -  theta1 = angle(Vr1);
12 -  deg1 = theta1 * (180/pi);
13
14 -  Zl2 = 2*pi*10000*0.01i;
15 -  Ze2 = (R*Zl2)/(R + Zl2);
16
17 -  Zc2 = -15.915i;
18
19 -  Vr2 = (Ze2)/(Zc2 + Ze2) * (2+0j);
20
21 -  M2 = abs(Vr2);
22 -  theta2 = angle(Vr2);
23 -  deg2 = theta2 * (180/pi);
```

```
Editor - D:\MatlabWork\lab6For1uF.m
lab6For1uF.m x +
24
25 -   t = 0:0.000001:0.003;
26 -   f1 = 1000;
27 -   f2 = 10000;
28 -   w1 = 2*pi*f1;
29 -   w2 = 2*pi*f2;
30 -   Vr1 = M1*sin(w1*t + deg1);
31 -   Vr2 = M2*sin(w2*t - deg2);
32 -   Vr = Vr1 + Vr2;
33
34 -   subplot(311)
35 -   plot(t,Vr1)
36 -   grid on
37 -   title('Source one only')
38
39 -   subplot(312)
40 -   plot(t,Vr2)
41 -   grid on
42 -   title('Source two only')
43
44 -   subplot(313)
45 -   plot(t,Vr)
46 -   grid on
47 -   title('Both Sources')
```


CODE OUTPUT:

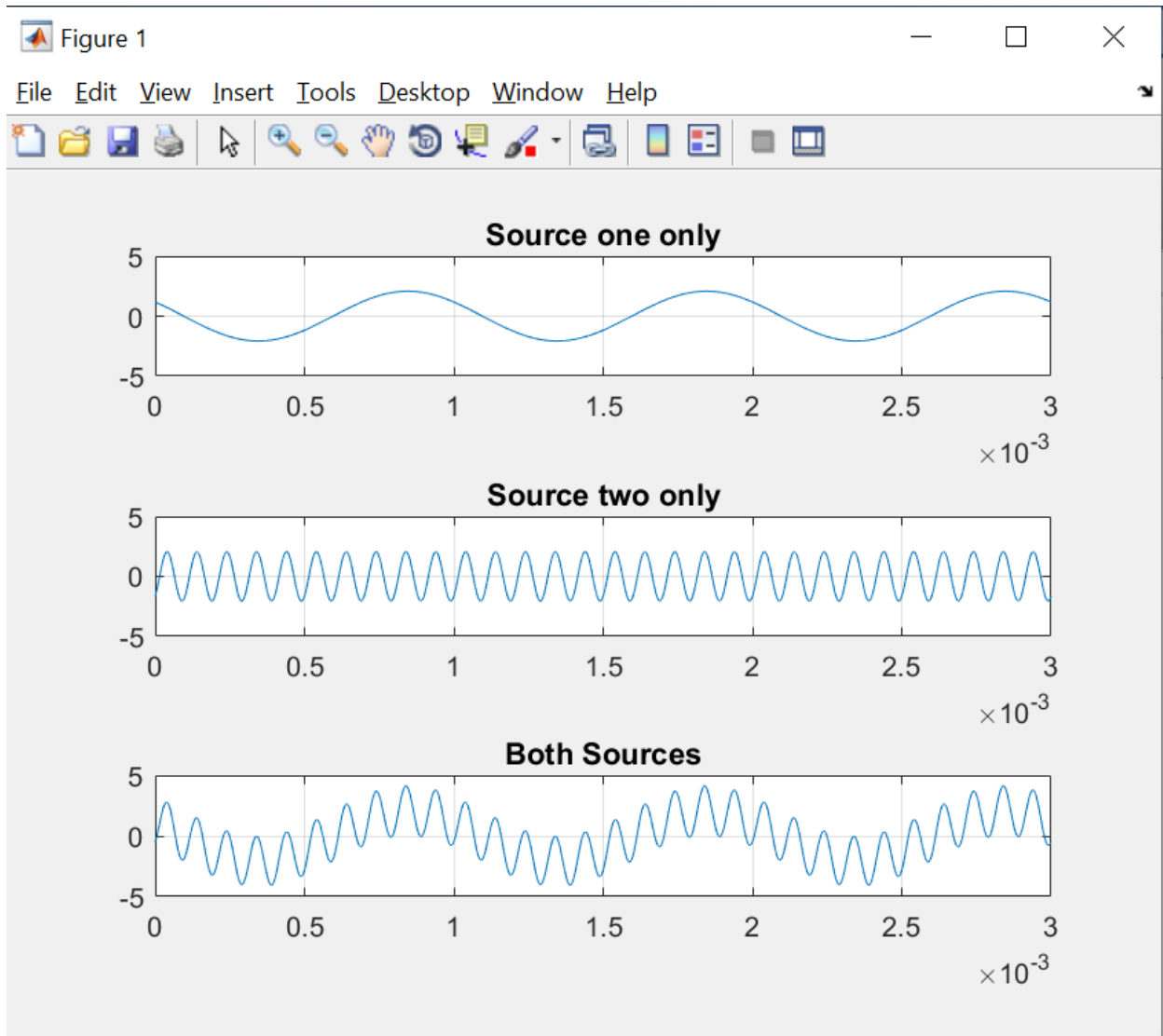

SOURCE 1 ONLY:

Table 1

	Theoretical	Experimental	%Deviation
V_R	2 V	2.2 V	%

SOURCE 2 ONLY:

Table 2

	Theoretical	Experimental	%Deviation
V_R	3 V	3.1 V	%

SOURCES 1 AND 2:

Table 3

	Theoretical	Experimental	%Deviation
V_R	5 V	5.1 V	%

ANSWERS OF QUESTIONS:

Q1: Why must the sources be replaced with a 50 Ω resistor instead of being shorted?

ANS: current flows in the least resistance path, for current to not flow in the path of second source when it is removed we short its path with appropriate resistance value which in this case, which in this case is 50 Ω .

Q2: Do the expected maxima and minima from step 6 match what is measured in step 7?

ANS: No. They don't.

Q3: Does one source tend to dominate the 1k Ω resistor voltage or do both sources contribute in nearly equal amounts? Will this always be the case?

ANS: Clearly from the table 1 and 2, the ac source with greater frequency (10k Hz) dominate over less frequency (1k Hz) source in spite of having same peak to peak voltage (2V) also the source with more peak-to-peak voltage will contribute more to the 1k resistor. They will equally contribute when both sources have same peak to peak voltage and frequency.

CONCLUSION:

We can conclude the following results from this experiment:

- Superposition theorem can also be applied to AC Circuits
- In case of AC, as a result of superposition, the resulting amplitude of AC Sine wave is the sum of the individual waves due to single source.