

## Experiment No. 2: Diode Characteristics

### Objectives:

To study the characteristics of silicon and germanium diodes.

### Equipment:

DC power supply

Function Generator

Digital Multimeter (DMM)

### Components

Diodes: Silicon (D1N4002), Germanium (D1N4148)

Resistors:  $1k\Omega$ ,  $1M\Omega$

### Theory:

#### Diode:

A diode is a two-terminal electronic component that conducts current primarily in one direction; it has low resistance in one direction, and high resistance in the other.

#### Characteristics:

- Three important characteristics of a diode are,
- first of all, the forward voltage drops. Under a forward bias condition, this should be about 0.7 volts.
- Then there is the reverse voltage drop. In the reverse, when we reverse bias the diode the depletion layer widens and usually, the applied voltages are felt across the diode.
- Then there is the reverse breakdown voltage. Reverse voltage drop that will reverse current flow and, in most cases, destroy the diode.

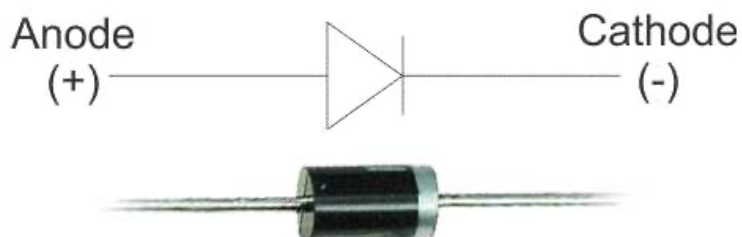


Figure 11 Diode

## **Function Generator**

A function generator is usually a piece of electronic test equipment or software used to generate different types of electrical waveforms over a wide range of frequencies. Some of the most common waveforms produced by the function generator are the sine, square, triangular and saw tooth shapes.



*Figure 2 Function Generator*

## **Power Supply**

A *power supply* is an electronic device that supplies electric energy to an electrical load. The primary function of a *power supply* is to convert one form of electrical energy to another and, as a result *power* supplies are sometimes referred to as electric *power* converters.



*Figure 3 DC Power Supply*

## **Digital Multimeter**

A digital multimeter (DMM) is a test tool used to measure two or more electrical values principally voltage (volts), current (amps) and resistance (ohms). It is a standard diagnostic tool for technicians in the electrical/electronic industries.

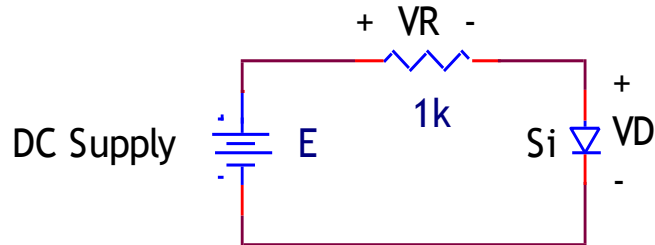


*Figure 4 Digital Multimeter*

## Procedure

### Part A: Forward-bias Diode Characteristics

1. Construct the circuit of *Fig. 3.1* with the supply ( $E$ ) is set at 0 V. Record the measured value of the resistor.

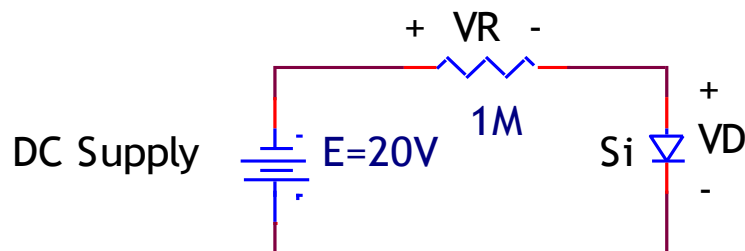


*Fig. 3.1*

2. Increase the supply voltage until  $V_D$  reads 0.1 V. Then measure current  $I_D$  and record the results in Table 3.1
3. Repeat step 2 for the remaining settings of  $V_D$  shown in the Table 3.1.  
Plot on a graph paper  $I_D$  versus  $V_D$  for the silicon. Complete the curves by extending the lower region of each curve to the intersection of the axis at  $I_D = 0$  mA and  $V_D = 0$  V.

### Part B: Reverse-bias Diode Characteristics


1. Construct the circuit of *Fig. 3.2* with  $E$  is set at 20V. Record the measured value of the resistor.



*Fig. 3.2*

2. Measure the voltage  $V_D$ . Measure the reverse saturation current,  $I_s$ .

### Results and Calculations:

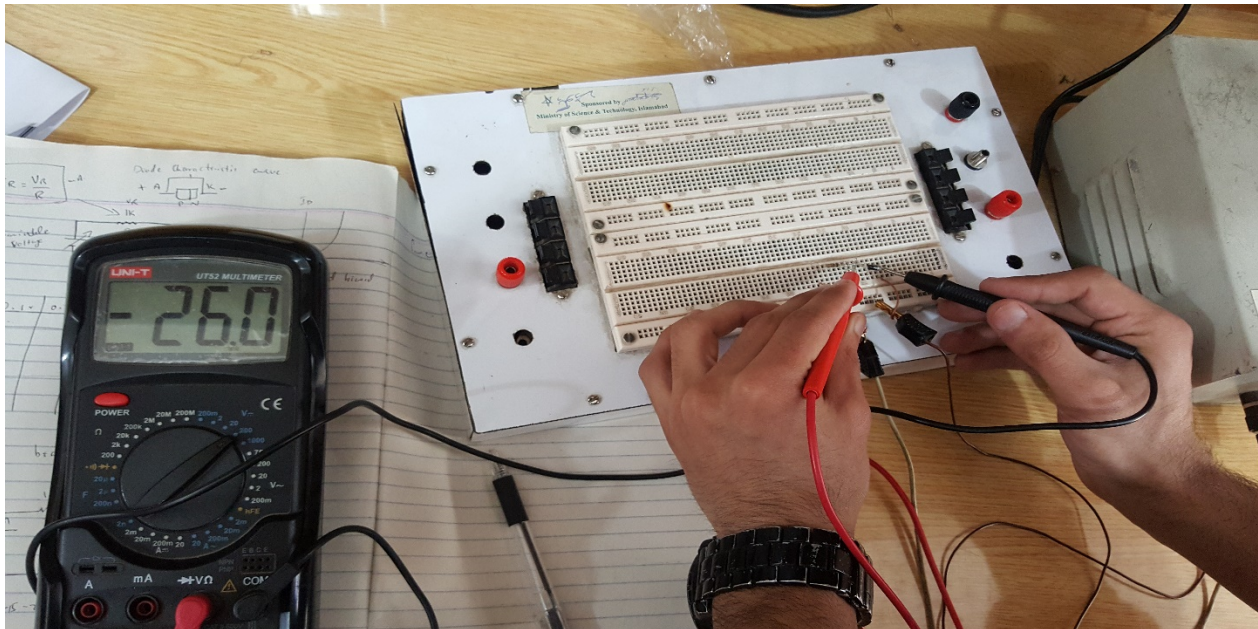

### Part A (Forward Bias):

$R$  (measured) =  $1k\ \Omega$

$I_D$  (measured). Fill in Table 3.1

$V_D$ (V)	0.13	0.21	0.37	0.42	0.51	0.60
$V_R$ (V)	0.5 mV	0.7 mV	14.5 mV	26.2 mV	2V	12.72V
$I_D$ (mA)	0.0005mA	0.0007mA	0.0145mA	0.0262mA	2mA	12.72mA

Table 3.1(Silicon Diode)

### Part B (Reverse Bias):

$R$  (measured) =  $1M\ \Omega$

#### Silicon Diode

$V_D$ (V)	-10.77	-15.21	-20.8	-25.0
$V_R$ (V)	-4.3 mV	-5.3 mV	-5.6 mV	-5.9 mV

$I_D$ (nA)	-4.3 nA	-5.3 nA	-5.6 nA	-5.9 nA
---------------	---------	---------	---------	---------

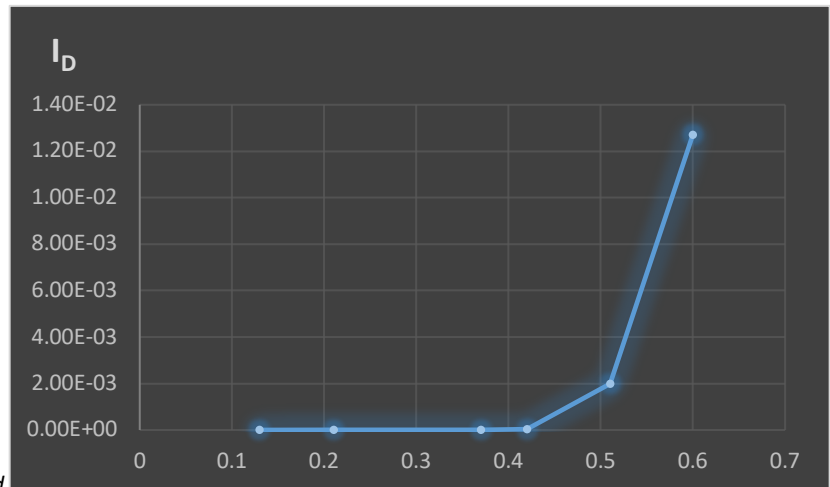


Figure 4 Forward Biased

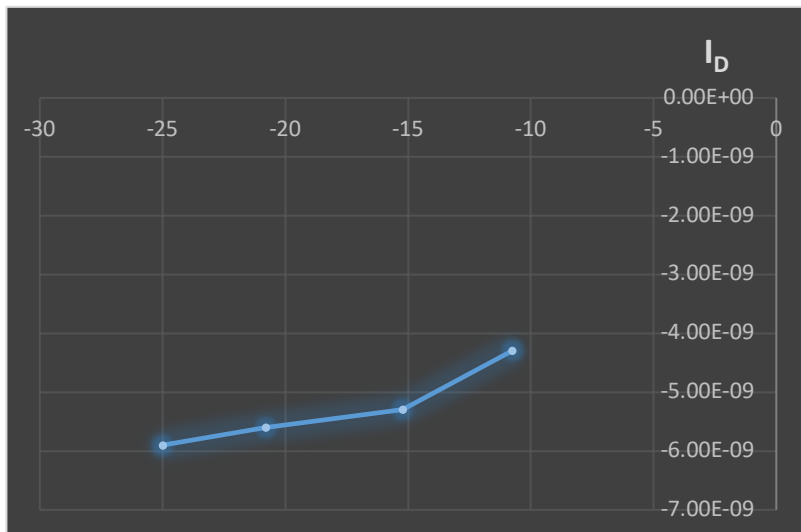


Figure 5 Reverse Biased

### Conclusion:

Hence, we practically observed the characteristics of diode in both forward and reversed biased using digital multimeter. In forward biased we saw the gradual increase in current  $I_D$  with the increase in voltage  $V_D$ . whereas in reverse biased we selected  $V_D$  from -10.77V to -25.0V on which we got the values of current  $I_D$  from -4.3 nA to -5.9 nA.

---