

## Experiment No. 4: Diode as Rectifier

### Objectives:

To become familiar with Full wave and Half wave rectification.

### Equipment:

Oscilloscope

Function Generator

Digital Multimeter (DMM)

### Components

Diodes: Silicon (D1N4002)

Resistor: 2.2 k $\Omega$ ,

### Theory:


#### **Diode:**

A diode is a two-terminal electronic component that conducts current primarily in one direction; it has low resistance in one direction, and high resistance in the other.

A widely used application of this feature and diodes in general is in the conversion of an alternating voltage (AC) into a continuous voltage (DC). In other words, *Rectification*.


Power diodes can be used individually as above or connected together to produce a variety of rectifier circuits such as “Half-Wave”, “Full-Wave” or as “Bridge Rectifiers”.

#### **Half Wave Rectification**

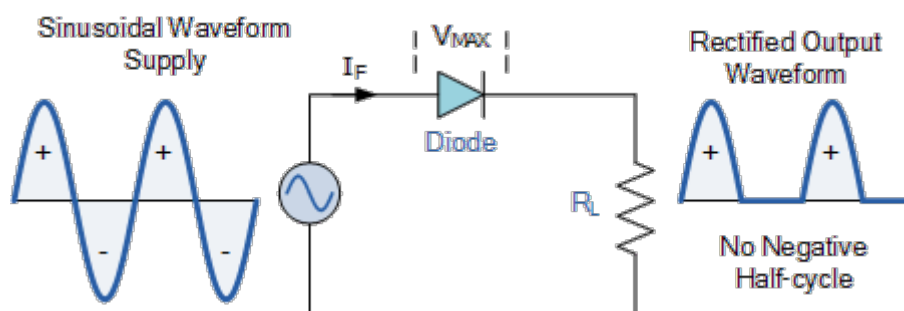


A rectifier is a circuit which converts the *Alternating Current* (AC) input power into a *Direct Current* (DC) output power. The input power supply may be either a single-phase or a multi-phase supply with the simplest of all the rectifier circuits being that of the **Half Wave Rectifier**.

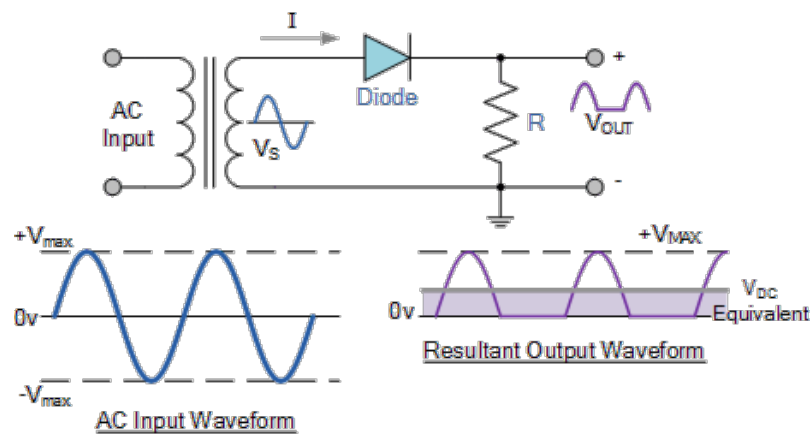The power diode in a half wave rectifier circuit passes just one half of each complete sine wave of the AC supply in order to convert it into a DC supply. Then this type of circuit is called a “half-wave” rectifier because it passes only half of the incoming AC power supply as shown.




## Full Wave Rectifier Circuit

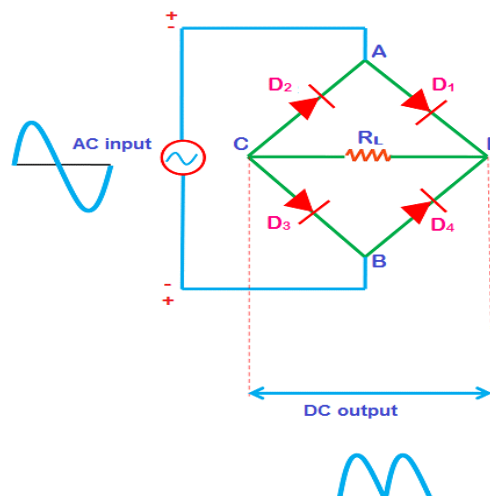


The full wave rectifier circuit consists of two *power diodes* connected to a single load resistance ( $R_L$ ) with each diode taking it in turn to supply current to the load. When point A of the transformer is positive with respect to point C, diode  $D_1$  conducts in the forward direction as indicated by the arrows.

When point B is positive (in the negative half of the cycle) with respect to point C, diode  $D_2$  conducts in the forward direction and the current flowing through resistor  $R$  is in the same direction for both half-cycles. As the output voltage across the resistor  $R$  is the phasor sum of the two waveforms combined, this type of full wave rectifier circuit is also known as a “bi-phase” circuit.

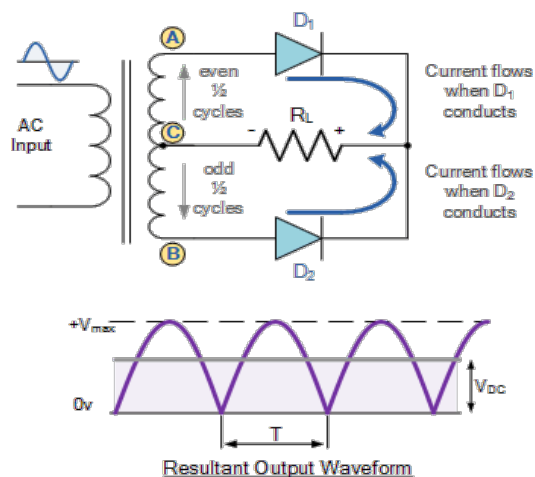


## Procedure

### Part 1

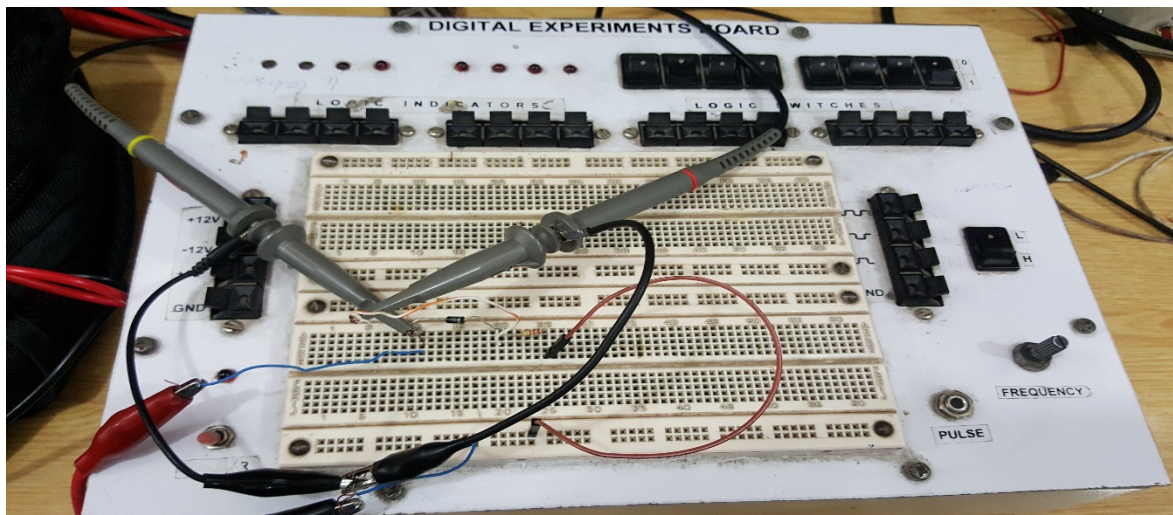

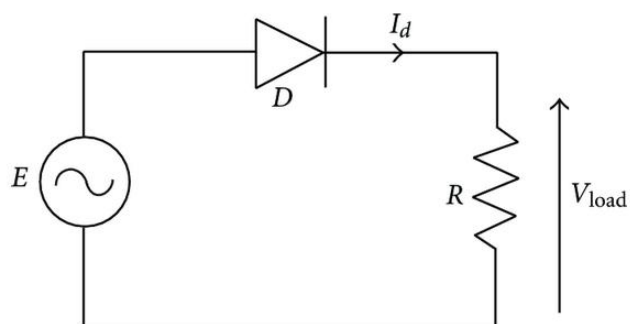1. Construct the circuit of *Fig* . Record the measured values as well as calculated values.



### Results:


#### **Calculated:**

$$V_T = 0.49 \text{ V}$$

$$\text{Voltage } V_D = \frac{V_m - V_T}{\pi} = \frac{4 - 0.49}{\pi} = 1.117 \text{ V}$$


#### **Measured:**

$$\text{Voltage } V_D = 1 \text{ V}$$

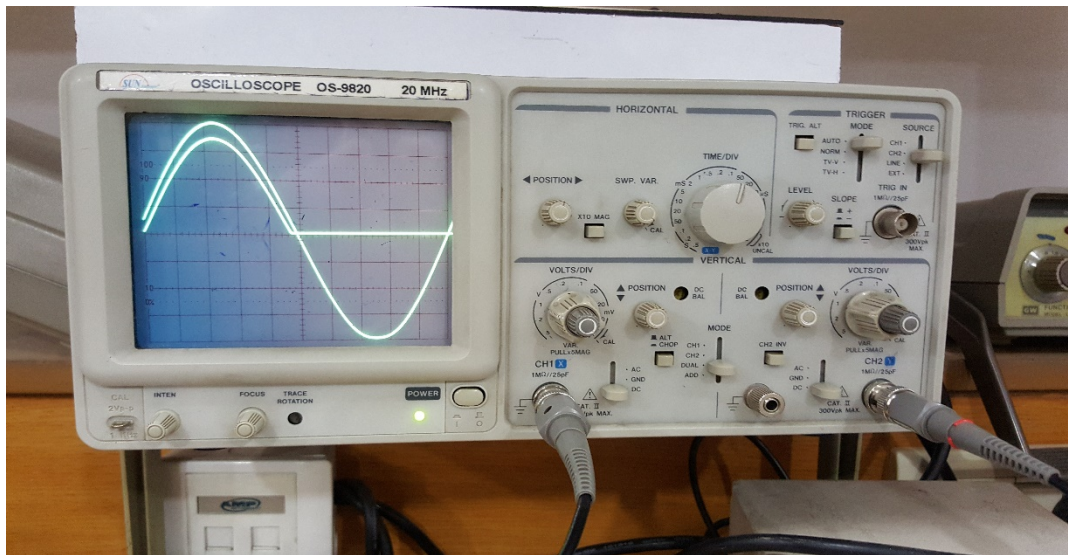
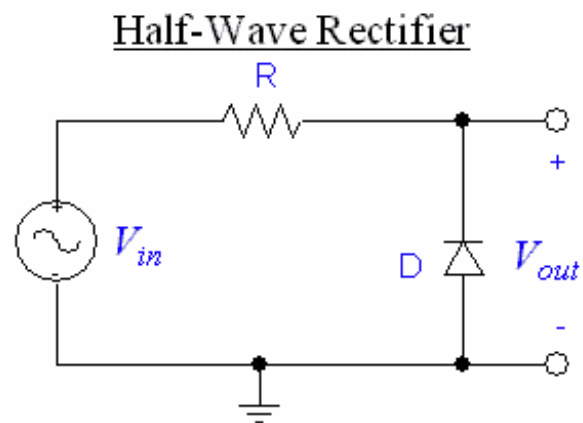
## Part 2:

Construct the circuit of Fig . Record the measured values as well as calculated values.



## Results:


### Calculated:

Voltage  $V_{T1} = 0.51 \text{ V}$

$$\text{Voltage } V_D = \frac{\text{Total Area}}{2\pi} = \frac{V_m}{\pi} - \frac{V_t}{2} = 0.945 \text{ V}$$


### Measured:

Voltage  $V_D = 0.93 \text{ V}$

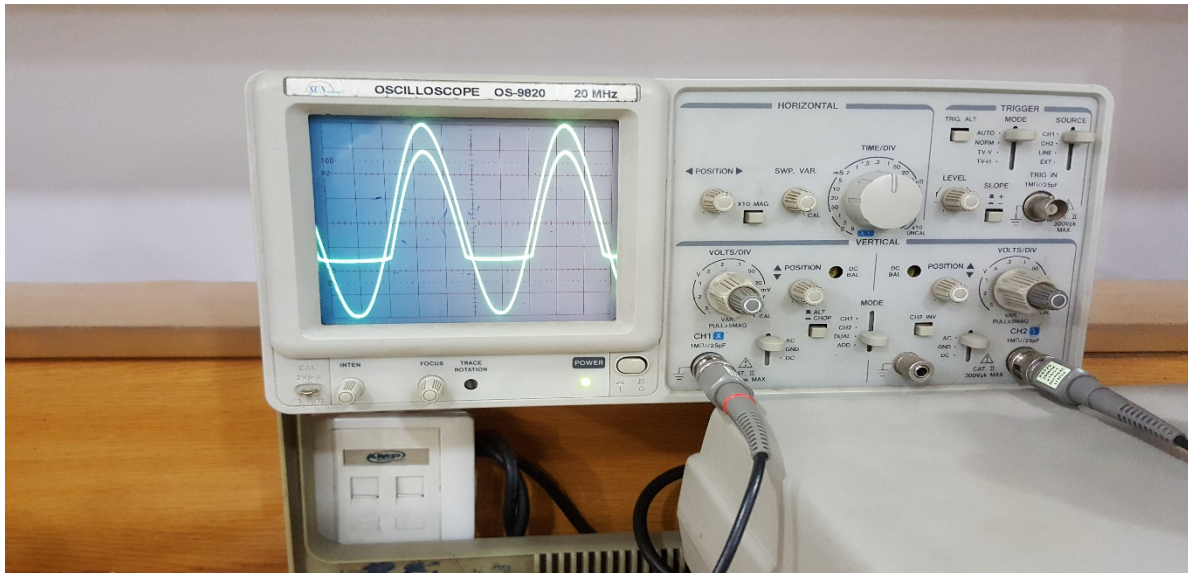
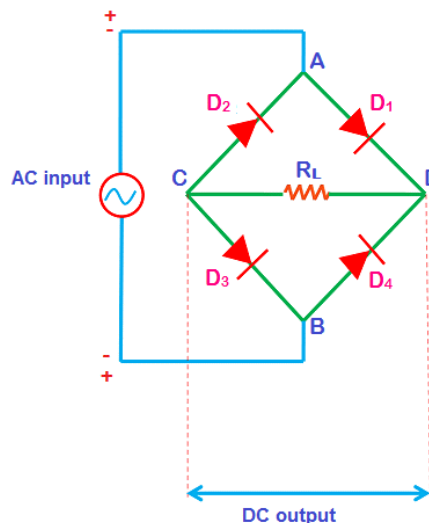
### Part 3:

- Construct the circuit of Fig. Record the measured as well as calculated values.



### Results:

#### Calculated:


$$\text{Voltage } V_T = \frac{V_{T1} + V_{T2} + V_{T3} + V_{T4}}{4} = 0.495 \text{ V}$$

$$\text{Resistance } R = 2.2 \text{ k}\Omega$$

$$\text{Voltage } V_D = \frac{2}{\pi} (V_m - 2V_T) = 0.636 (4 - 2(0.495)) = 1.91 \text{ V}$$

#### Measured:

$$\text{Voltage } V_D = 1.58 \text{ V}$$

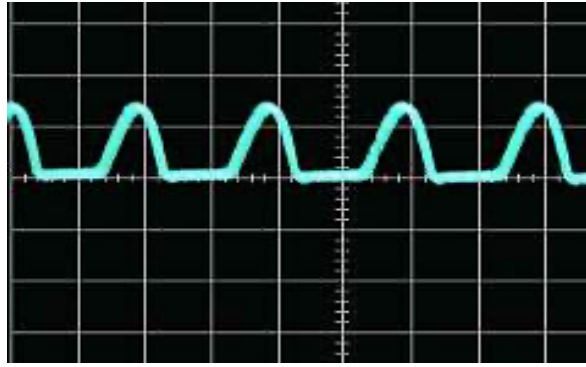

### Percentage Error:

$$(V_{DC} \text{ Cal} - V_{DC} \text{ Measured} / V_{DC} \text{ Cal}) \times 100 = 17.7 \%$$

---

### Conclusion:

Hence, we practically observed the behavior of diodes as rectifiers.

- In half wave rectification we saw that only half of every cycle of an alternating current is made to flow in one direction only.
  - In full wave rectification we saw that it converted both half cycles of the AC signal into pulsating DC signal.
-