



LAB # 8

CSE-202L Digital Logic Design Lab

Fall 2022

SUBMITTED BY:

Ali Asghar(21PWCSE2059)
Suleman Shah(21PWCSE1983)
Abu Bakar(21PWCSE2004)

DATED:

7th January, 2023

SUBMITTED TO:

Engr. Rehmat Ullah

Lab # 8: Magnitude comparators

Objective: · Realization of 1-bit comparator using

logic gates.

Realization and implementation of 2-bit comparator using logic gates on breadboard. · Implementation of 4-bit magnitude comparator on breadboard using IC 7485.

Components Required:

- Breadboard.
- IC Type 7486 Quadruple 2-input XOR gates.
- IC Type 7408 Quadruple 2-input AND gates.
- IC Type 7400 Quadruple 2-input NAND gates.
- IC Type 7410 Triple 3-input NAND gates.
- IC Type 74L85 4-bit magnitude comparator.
- Switches for inputs and
- LED displays for outputs.

Theory:

Magnitude comparator is a combinational logic circuit that compares between two binary numbers A and B and determines their relative magnitudes. The output of the circuit is specified by three binary variables whether: $A > B$, $A = B$ or $A < B$.

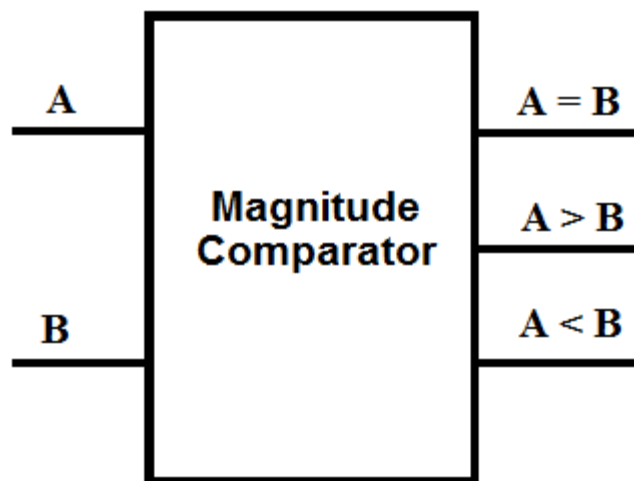


Figure 1: Block diagram of n-bit MagnitudComparator.

1-bit Magnitude Comparator:


A comparator used to compare two 1-bit binary numbers. It has two binary inputs A, B and three binary outputs: greater than, equal and less than relations. Figure 2 below shows the block diagram and truth table of a 1-bit magnitude comparator.

(b) Truth table

1

Inputs		Outputs		
B	A	$A > B$	$A = B$	$A < B$
0	0	0	1	0
0	1	1	0	0
1	0	0	0	1
1	1	0	1	0

(a) Block diagram

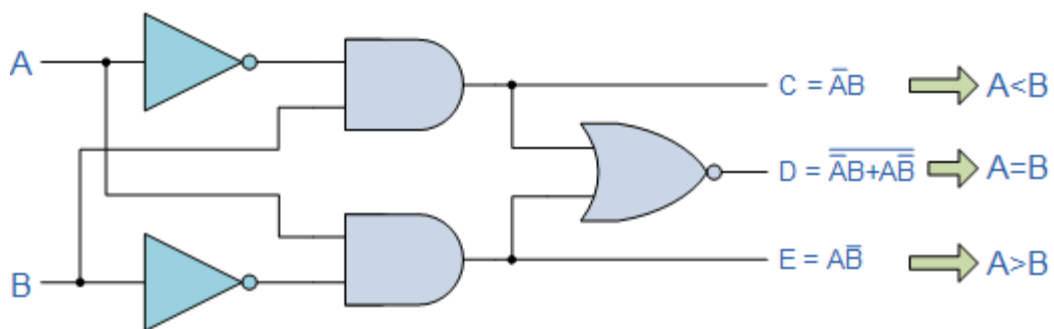

The Boolean functions describing the 1-bit magnitude comparator according to the truth table are: $(A > B)$


$= A'B (A = B) = A'B' + AB = B \oplus A$)'($A < B$) = AB' The logic diagram for 1-bit binary comparator implemented by XOR and basic logic gates is shown below in figure 3.

So we conclude that digital comparators actually use **Exclusive-NOR** gates within their design for comparing their respective pairs of bits.

2-bit Magnitude Comparator


A comparator used to compare two 2-bit numbers. It has 4 binary inputs number A: A_1A_0 , number B: B_1B_0) and 3 binary outputs: greater than, equal and less than relations. Figure 4 below shows the block diagram and truth table of a 2-bit magnitude comparator.

Inputs				Outputs		
A_1	A_0	B_1	B_0	$A > B$	$A = B$	$A < B$
0	0	0	0	0	1	0
0	0	0	1	0	0	1
0	0	1	0	0	0	1
0	0	1	1	0	0	1
0	1	0	0	1	0	0
0	1	0	1	0	1	0
0	1	1	0	0	0	1
0	1	1	1	0	0	1
1	0	0	0	1	0	0
1	0	0	1	1	0	0
1	0	1	0	0	1	0
1	0	1	1	0	0	1
1	1	0	0	1	0	0
1	1	0	1	1	0	0
1	1	1	0	1	0	0
1	1	1	1	0	1	0

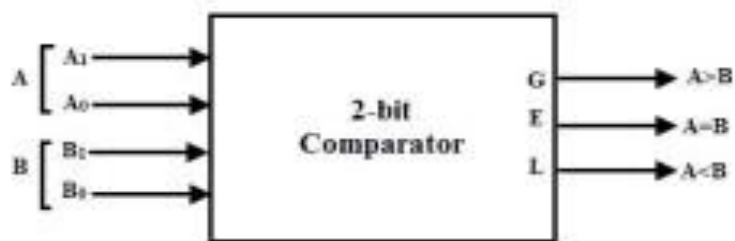

(a)Block diagram (b) Truth table

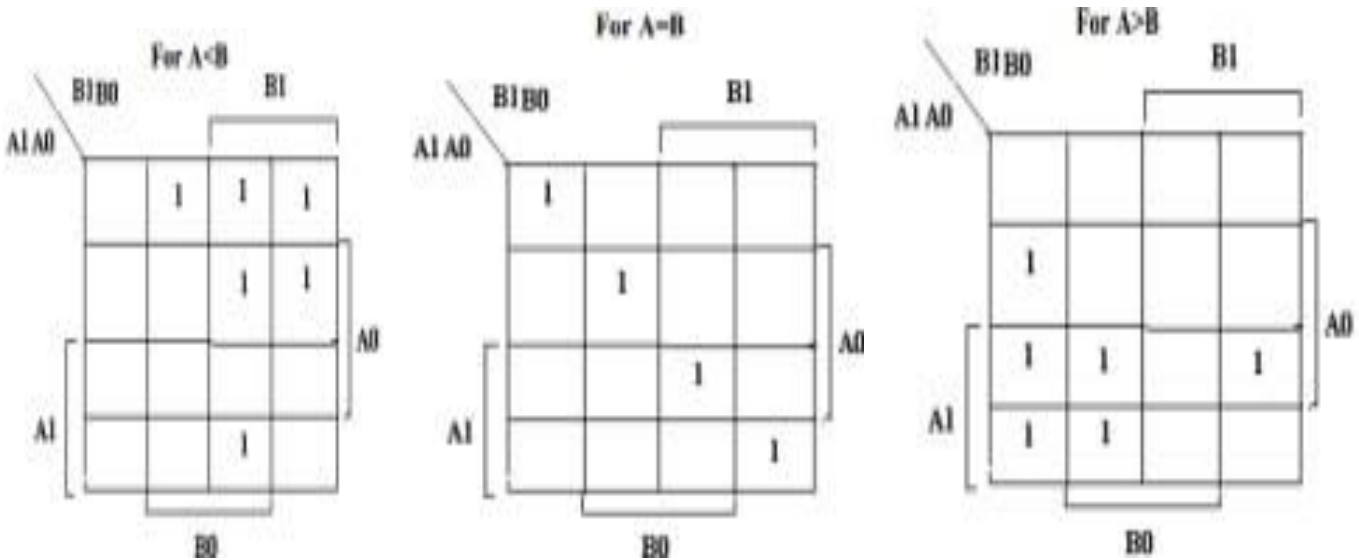Using key-map, the simplified Boolean function for the outputs $A > B$, $A = B$ and $A < B$ is shown below:



$A=B$:

$$\begin{aligned}
 &= A_1' A_0' B_1' B_0' + A_1' A_0 B_1' B_0 + \\
 &A_1 A_0' B_1 B_0' + A_1 A_0 B_1 B_0 = (A_1' B_1' + A_1 B_1) (A_0' B_0' + A_0 B_0) = \\
 &(A_1 \oplus B_1)' (A_0 \oplus B_0)' \\
 &= X_1 X_0
 \end{aligned}$$

$A>B$:

$$\begin{aligned}
 &= A_1 B_1' + A_1' A_0 B_1' B_0' + A_1 A_0 B_1 B_0' \\
 &= A_1 B_1' + A_0 B_0' (A_1' B_1' + A_1 B_1) = \\
 &A_1 B_1' + A_0 B_0' (A_1 \oplus B_1)' \\
 &= A_1 B_1' + X_1 A_0 B_0'
 \end{aligned}$$

$A<B$:

$$\begin{aligned}
 &= A_1' B_1 + A_1' A_0' B_1' B_0 + A_1 A_0' B_1 B_0 \\
 &= A_1' B_1 + A_0' B_0 (A_1' B_1' + A_1 B_1) = \\
 &A_1' B_1 + A_0' B_0 (A_1 \oplus B_1)' = A_1' B_1 + X_1 A_0' B_0
 \end{aligned}$$

2 Based on the simplified Boolean functions for the three outputs $A > B$, $A = B$ and $A < B$, the logic diagram of the 2-bit magnitude comparator is shown below:


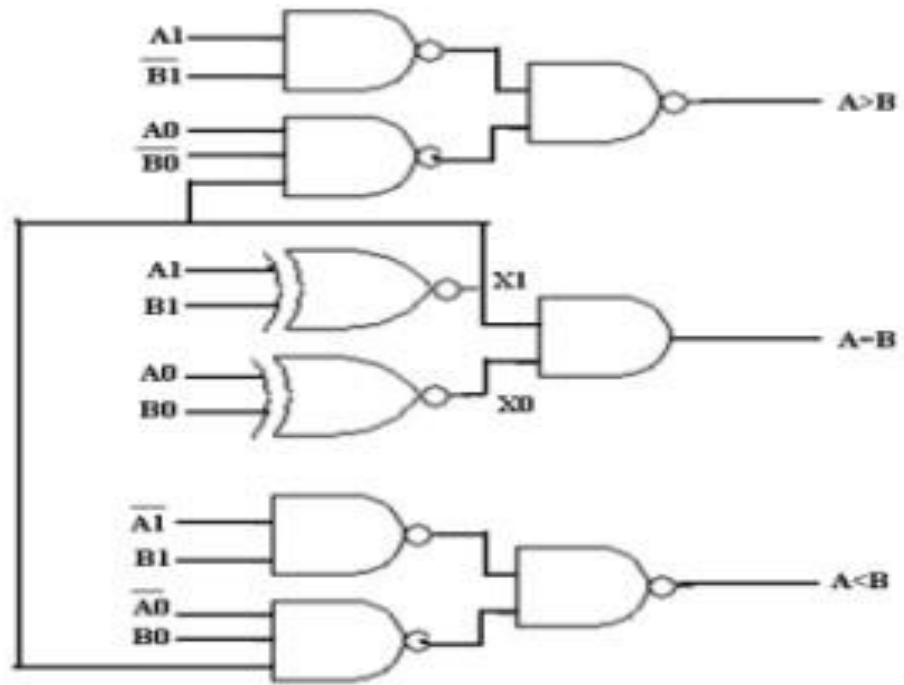
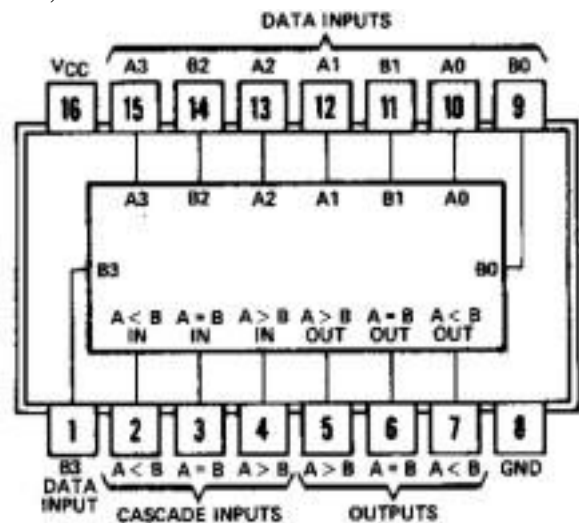


Figure 5: Logic Diagram of 2-bit Comparator

4-bit Magnitude Comparator:

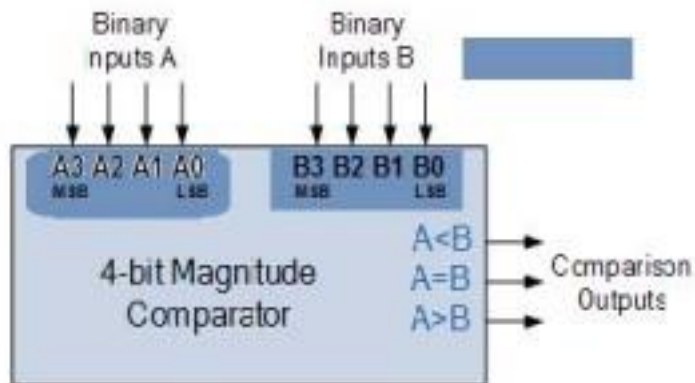A comparator used to compare two 4-bit words. The two 4-bit numbers are word A: $A_3 A_2 A_1 A_0$, and word B: $B_3 B_2 B_1 B_0$. So the circuit has 8 inputs and 3 binary outputs: $A > B$, $A = B$ and $A < B$.



(a)Block diagram (b) Pin description for IC 7485

Figure 6 shows the block diagram and pin configuration of IC 7485 for 4-bit magnitude comparator. Three inputs are available for cascading comparators.

This comparator generates an output of 1 at one of three comparison outputs such that:

- If word A is bigger than word B; $A > B$ output (pin 5) is “1”,
- If word A is smaller than word B; $A < B$ output (pin 7) is “1”,
- If word A is equal to word B; $A = B$ output (pin 6) is “1”.

3 This IC can be used to compare two 4-bit binary words by grounding the cascade inputs $A < B$ (pin 2) and $A > B$ (pin 4) and connecting the cascade input $A = B$ (pin 3) to V_{cc} .

How does a 4-bit comparator work?

Equality:

Word A equal word B iff: $A_3=B_3, A_2=B_2, A_1=B_1, A_0=B_0$.

Inequality:

- If $A_3 = 1$ and $B_3 = 0$, then A is greater than B ($A > B$). Or
- If A_3 and B_3 are equal, and if $A_2 = 1$ and $B_2 = 0$, then $A > B$. Or
- If A_3 and B_3 are equal & A_2 and B_2 are equal, and if $A_1 = 1$, and $B_1 = 0$, then $A > B$. Or · If A_3 and B_3 are equal, A_2 and B_2 are equal and A_1 and B_1 are equal, and if $A_0 = 1$ and $B_0 = 0$, then $A > B$.
- If $A_3 = 0$ and $B_3 = 1$, then A is less than B ($A < B$). Or
- If A_3 and B_3 are equal, and if $A_2 = 0$ and $B_2 = 1$, then $A < B$. Or
- If A_3 and B_3 are equal & A_2 and B_2 are equal, and if $A_1 = 0$, and $B_1 = 1$, then $A < B$. Or · If A_3 and B_3 are equal, A_2 and B_2 are equal and A_1 and B_1 are equal, and if $A_0 = 0$ and $B_0 = 1$, then $A < B$.


Part A: Lab Tasks

Procedure:


1. Check all the components for their working.
2. Insert the appropriate ICs into the IC base.
3. Make connections as shown in the circuit diagram in figure 5.
4. Verify the Truth Table and observe the outputs.
5. Repeat the same steps but for the circuit diagram in figure 6 and apply inputs in the following table.
Record the outputs for the given values of A and B.

Inputs		Outputs		
A	B	$A < B$	$A = B$	$A > B$
00001100	00001100	0	1	0
00001010	00010001	1	0	0
00001111	00000101	0	0	1
00011000	00011000	0	1	0

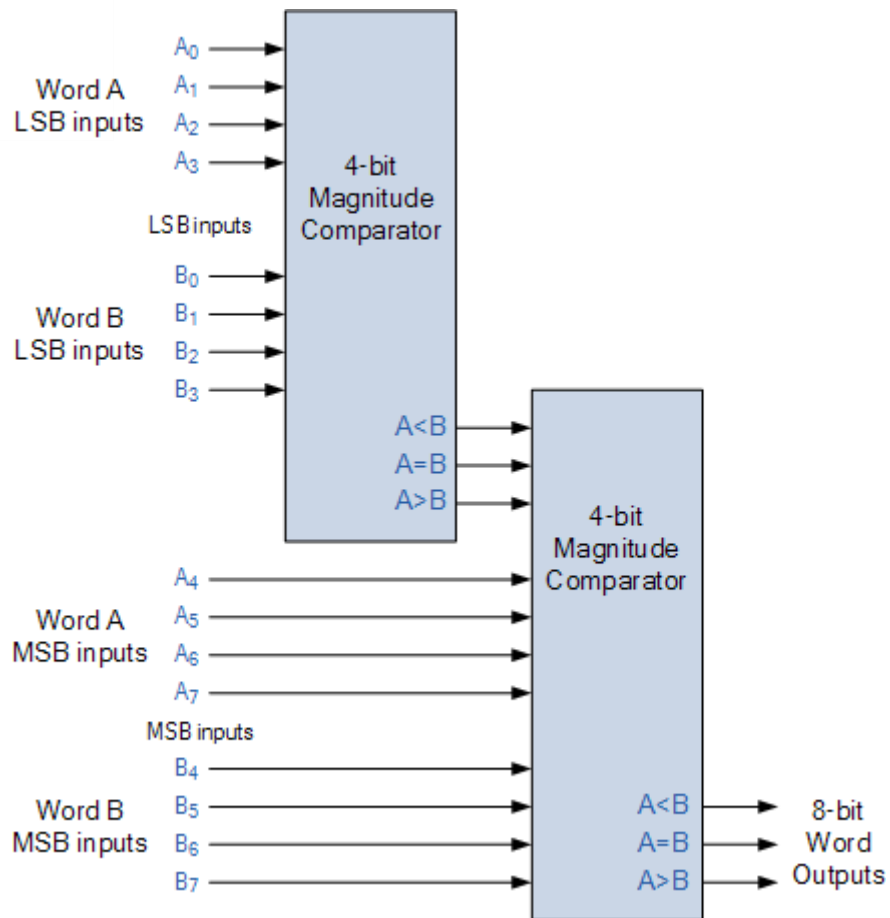
Design an 8-bit comparator using two chips of IC 7485. The connections are given below. 2.
Verify the given truth table.



PIN DIAGRAM FOR IC 7485

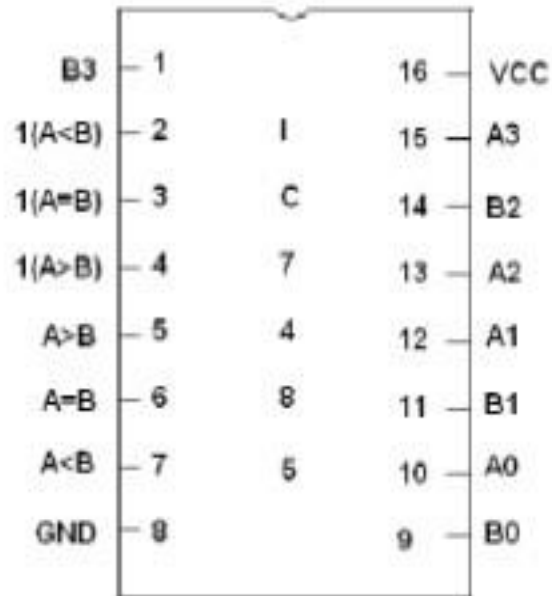


LOGIC DIAGRAM 8 BIT MAGNITUDE COMPARATOR

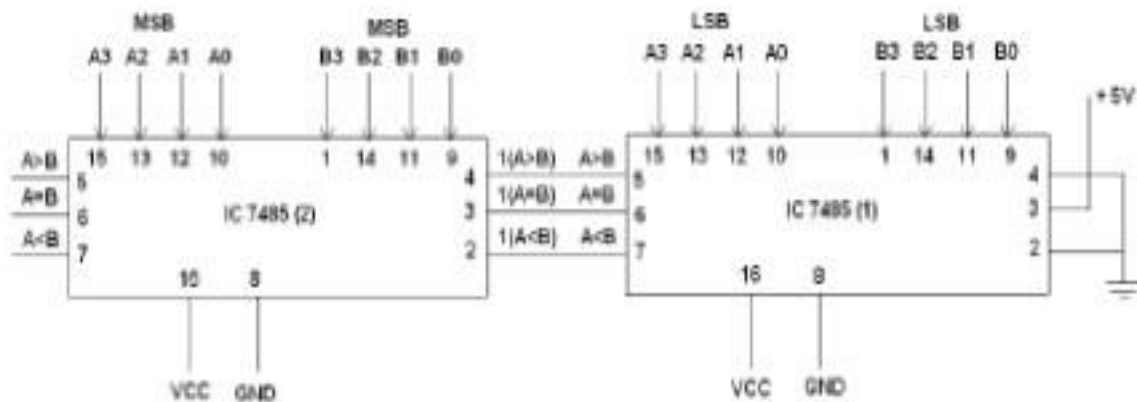


TRUTH TABLE


A		B		A>B	A=B	A<B
0000	0000	0000	0000	0	1	0
0001	0001	0000	0000	1	0	0
0000	0000	0001	0001	0	0	1

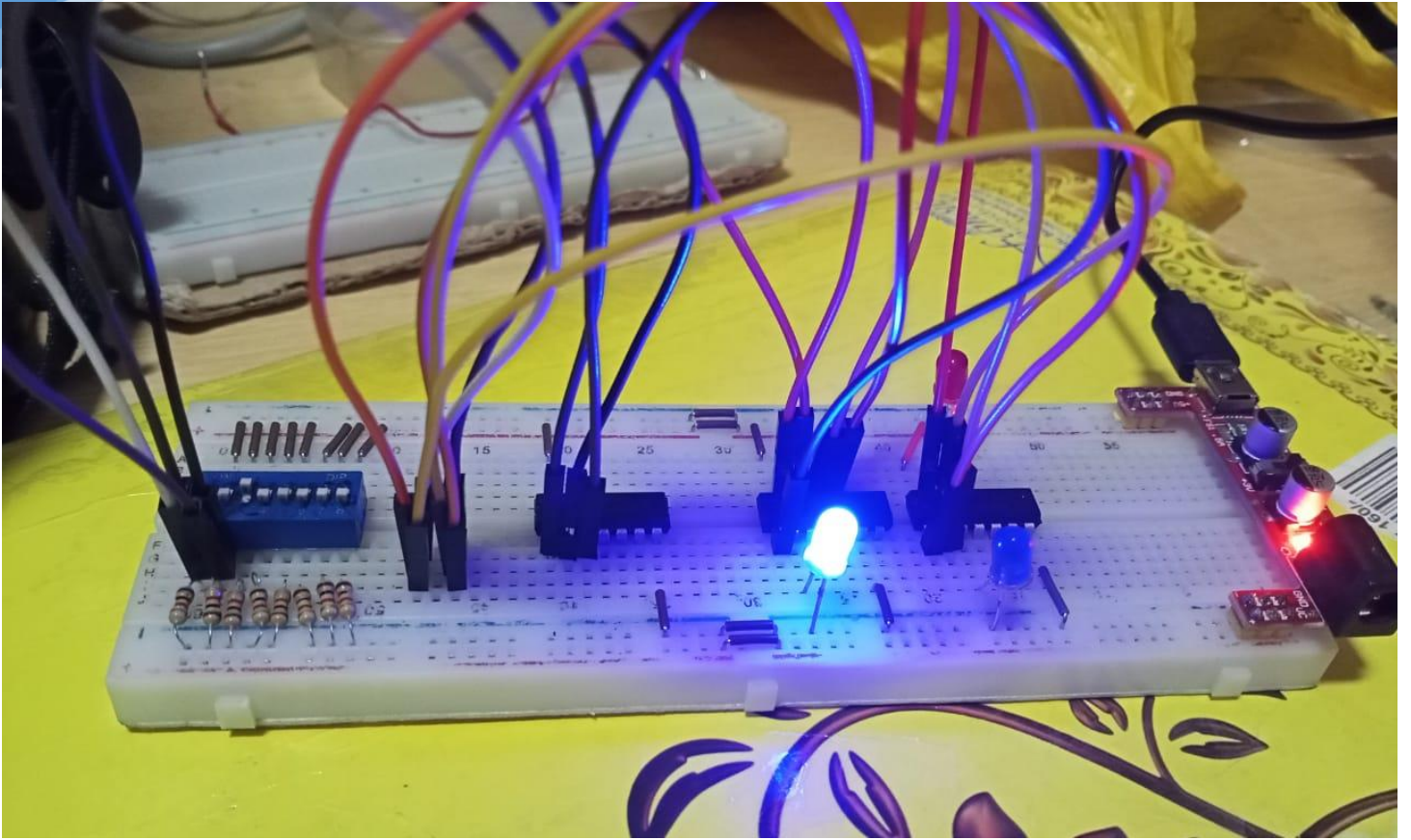


1 Bit Comparator

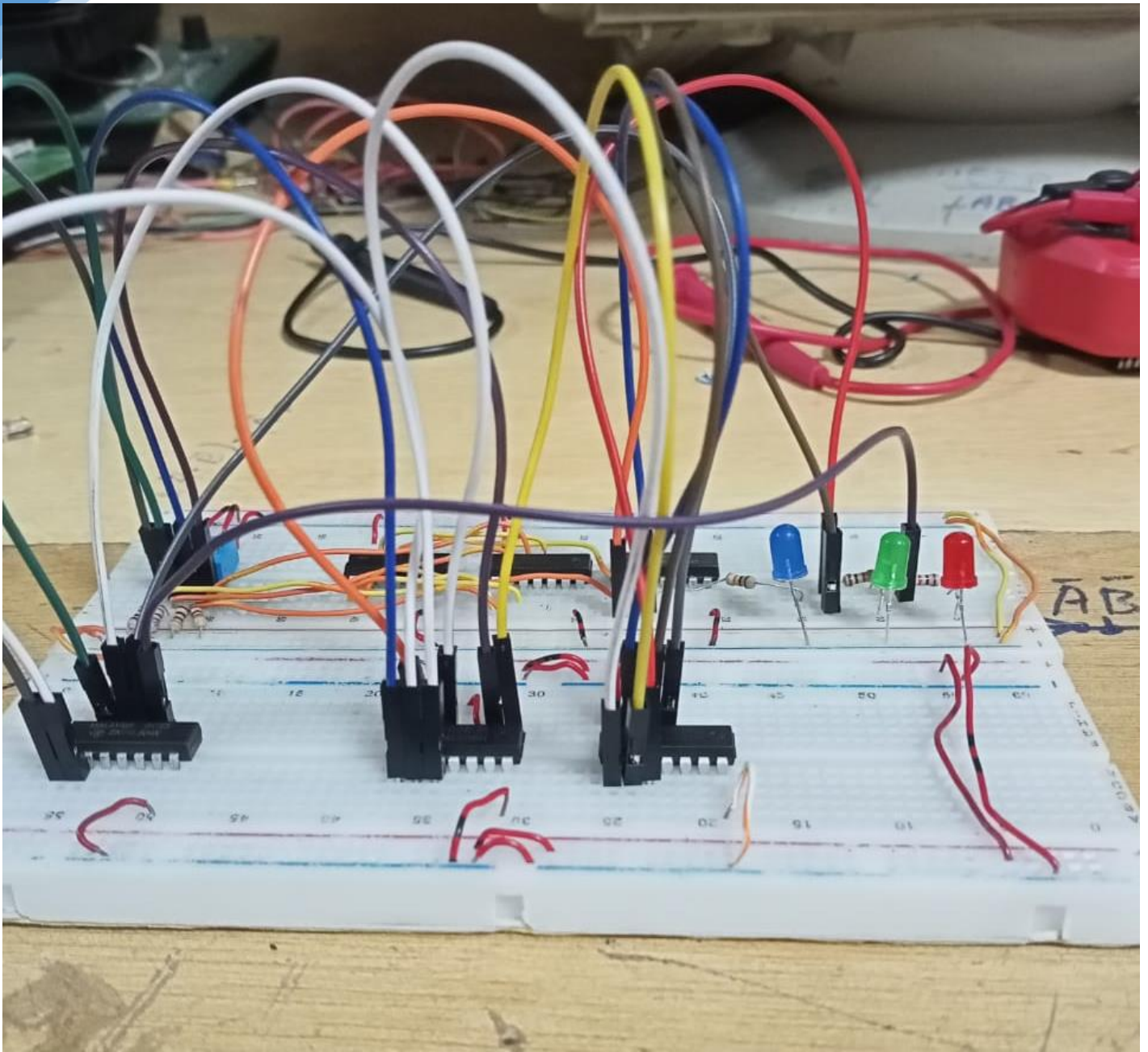

2 Bit Comparator

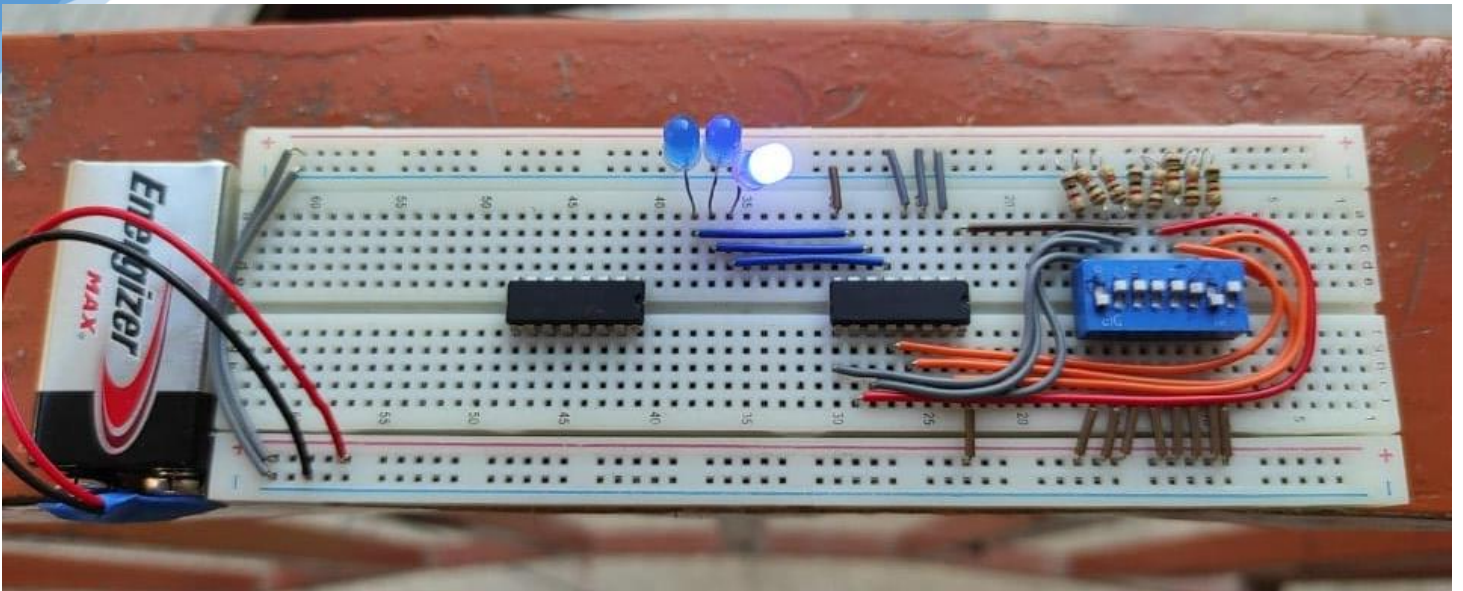

4 Bit Comparator

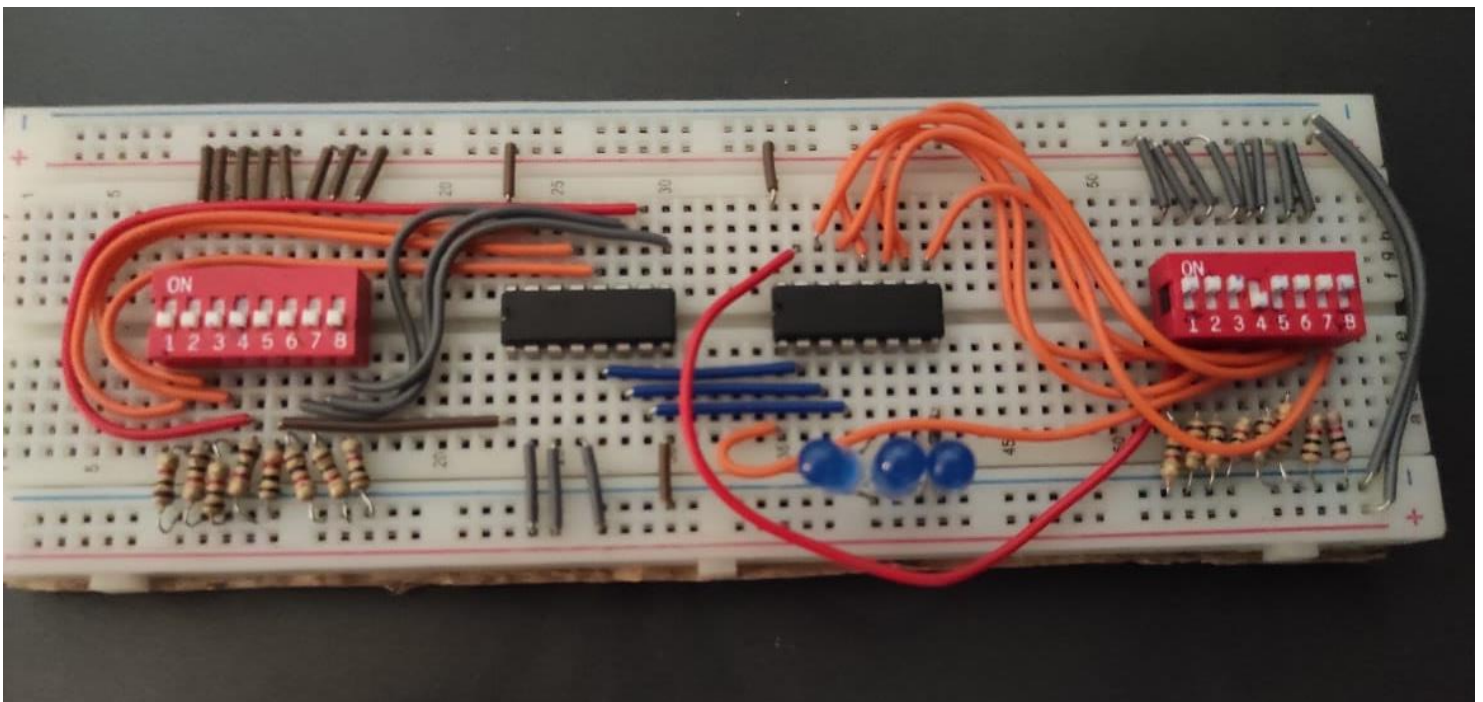

8 Bit Comparator