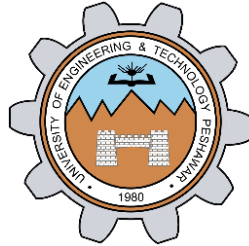


LAB # 9



CSE-203L Circuit & Systems-II Lab

Fall 2022

Submitted by: Ali Asghar

Registration No.: 21PWCSE2059

Class Section: C

“On my honor, as student of University of Engineering and Technology, I have neither given nor received unauthorized assistance on this academic work.”

Student Signature: _____

Submitted to:

Engr. Faiz Ullah

20th December, 2022

Department of Computer Systems Engineering
University of Engineering and Technology, Peshawar

TITLE:

Operational Amplifier as Integrator

OBJECTIVES:

- To learn how to use the operational amplifier as an integrator

APPARATUS:

- Oscilloscope
- AC Function Generator

COMPONENTS:

- 10k Ω & 22K Ω Resistors
- 0.1 μ F Capacitor
- LM 741 Op-Amp

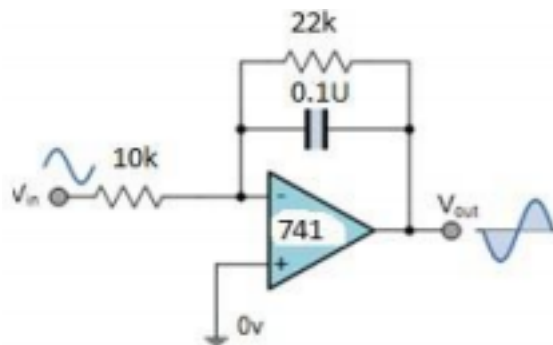
THEORY OVERVIEW:

Figure 2

PROCEDURE:

1. Connect the components/equipment as shown in the circuit diagram Figure 2.
2. Switch ON the power supply.
3. Apply sine wave at the input terminals of the circuit using function Generator.

4. Connect channel-1 of CRO at the input terminals and channel-2 at the output terminals.
5. Observe the output of the circuit on the CRO which is a cosine wave (90° phase shifted from the sine wave input) and note down the position, the amplitude and the time period of V_{in} & V_o .
6. Now apply the square wave as input signal.
7. Observe the output of the circuit on the CRO which is a triangular wave and note down the position, the amplitude and the time period of V_{in} & V_o .
8. Plot the output voltages corresponding to sine and square wave inputs as shown in the Figure 3 below.

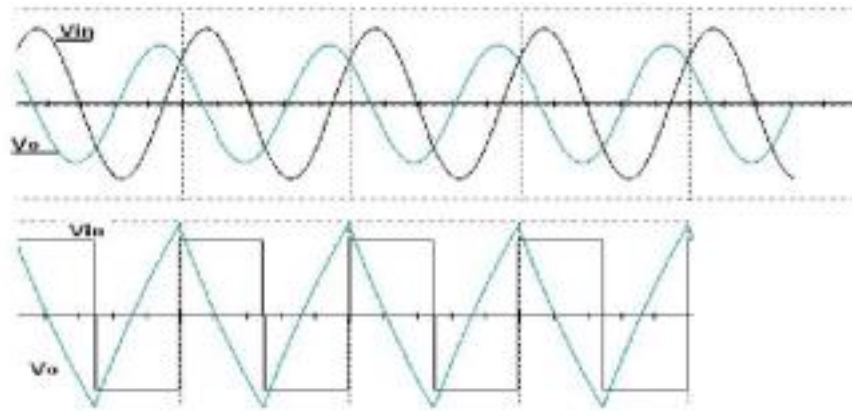


Figure 3


CALCULATIONS:

V_o can be calculated by the following formula.

$$V_o = \frac{1}{R_{in}C_f} \int V_{in} dt$$

By putting given values in above formula, we get the results shown in table on the next page.

OBSERVATIONS:

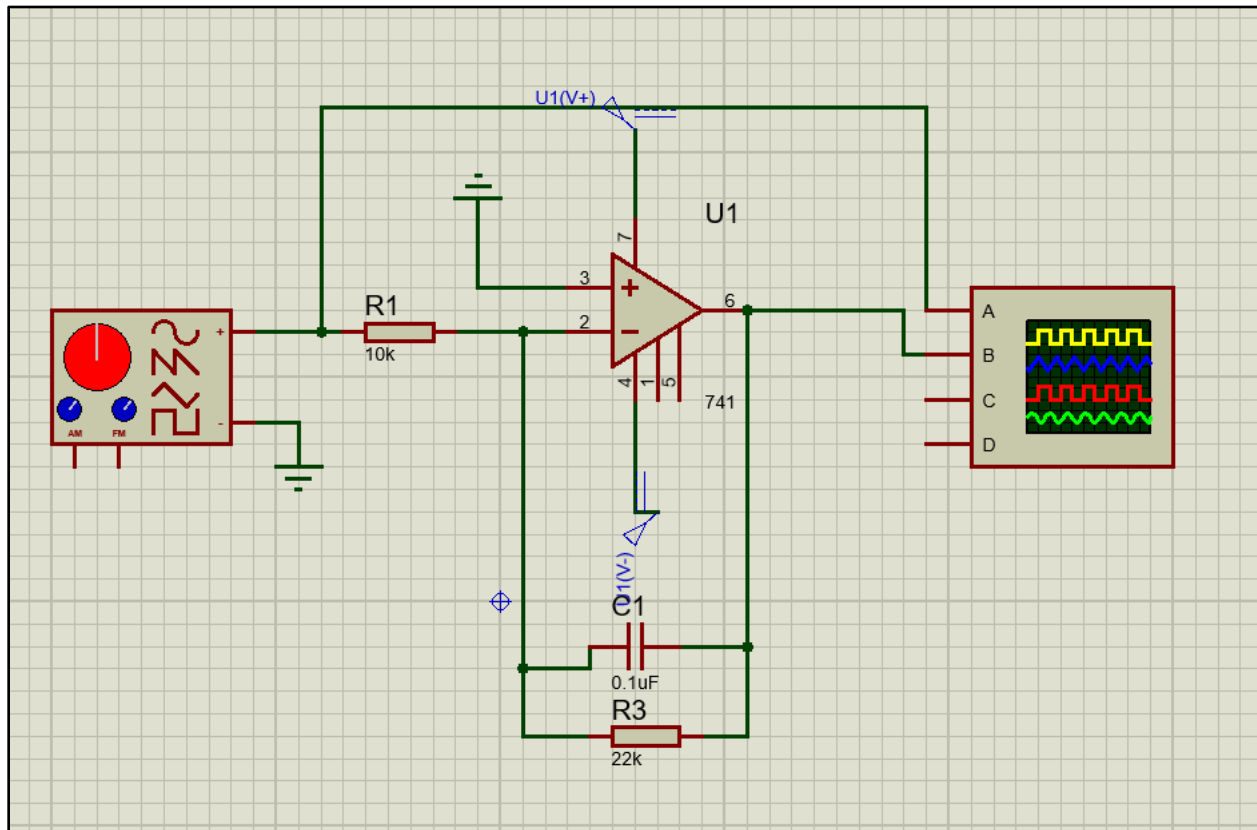

Op-Amp as an Integrator

$V_{in(p-p)}$	Frequency	V_o (Theoretical)	V_o (Experimental)	%Error
1V	1kHz	0.1592	0.1607	1%
2V	1kHz	0.3183	0.3201	0.55%
1V	2kHz	0.0796	0.0832	4.6%
2V	1.5kHz	0.2122	0.2147	1.19%
2.5V	2.5kHz	0.1592	0.1641	3.11%

CONCLUSION:

We conclude the following results from this experiment:

- **Op-amp Integrator** is an operational amplifier circuit that performs the mathematical operation of **Integration**
- By replacing this feedback resistance with a capacitor, we have an RC Network connected across the operational amplifiers feedback path producing another type of operational amplifier circuit commonly called an **Op-amp Integrator** circuit as shown below.