

LAB # 5

CSE-202L Digital Logic Design Lab

Fall 2022

SUBMITTED BY:

Ali Asghar(21PWCSE2059)

Suleman Shah(21PWCSE1983)

Abu Bakar(21PWCSE2004)

DATED:

11th November, 2022

SUBMITTED TO:

Engr. Rehmat Ullah

**Department of Computer Systems Engineering
University of Engineering & Technology, Peshawar**

ADDERS AND SUBTRACTORS

OBJECTIVES:

- To Design and construct half adder, full adder, half subtractor and full subtractor circuits
- Verify their truth tables using logic gates


COMPONENTS:

- IC's
 - 7408 Quad-2-Input AND Gate
 - 7432 Quad-2-Input OR Gate
 - 7486 Quad-2-Input XOR Gate
 - 7404 Hex Inverters
- LED's
- Dip Switch
- 520/1KΩ Resistors

THEORY:

A digital adder circuit adds binary signals & a subtractor subtracts binary signals. Half Adder/Subtractor is a basic circuit that adds / subtracts 2 bits and generates Sum or Difference along with Carry / Borrow. Unlike Half Adder or Subtractor a Full Adder / Subtractor has the provision to take consideration of previous Carry / Borrow also.


LOGIC DIAGRAM HALF ADDER

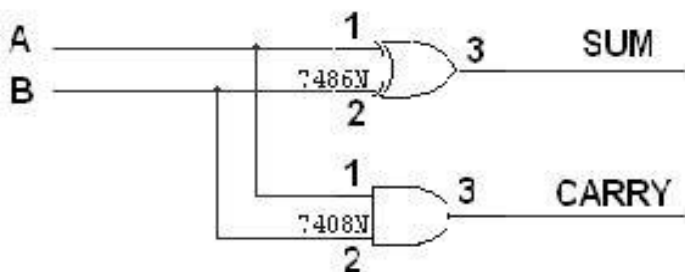

TRUTH TABLE

A	B	CARRY	SUM
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

$$\text{SUM} = A'B + AB'$$

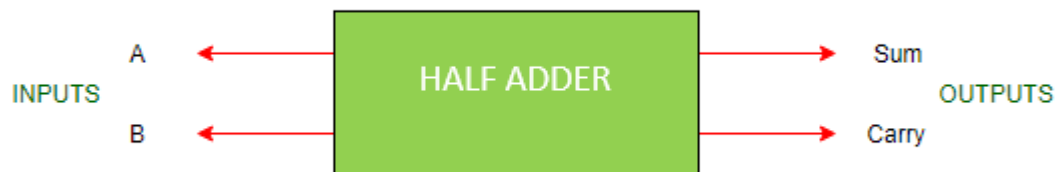

	B	0	1	
A				
0			1	$A'B$
1		1		$B'A$

$$A'B + B'A = A \text{ xor } B$$


$$\text{CARRY} = AB$$

		B	0	1
A				
0				
1			1	

→ AB

LOGIC DIAGRAM FULL ADDER:


FULL ADDER USING TWO HALF ADDER

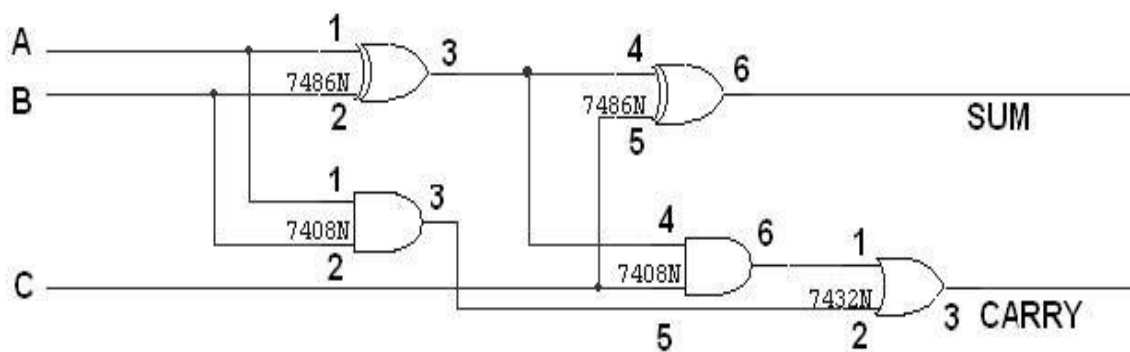

TRUTH TABLE

A	B	C	CARRY	SUM
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

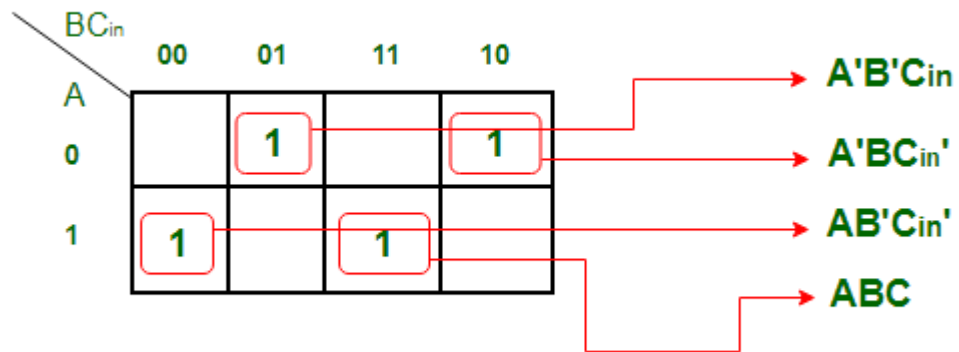
$$\text{SUM} = A'B'Y + A'BY' + ABY + AB'Y' = Y(A'B' + AB) + Y'(A'B + AB') = YX' + Y'X$$




$$\text{CARRY} = AB + BY + AY = Y(A+B) + AB$$

		BC _{in}			
		00	01	11	10
A	0			1	
	1		1	1	1

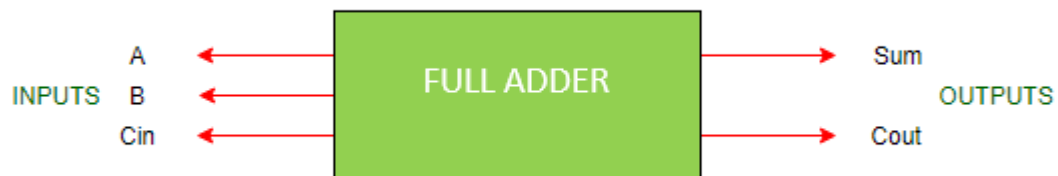The truth table shows the values of BC_{in}, AC_{in}, and AB for each combination of A and B. Red boxes highlight the values of BC_{in} (1), AC_{in} (1), and AB (1) for the input combination A=0, B=1.



LOGIC DIAGRAM HALF SUBTRACTOR

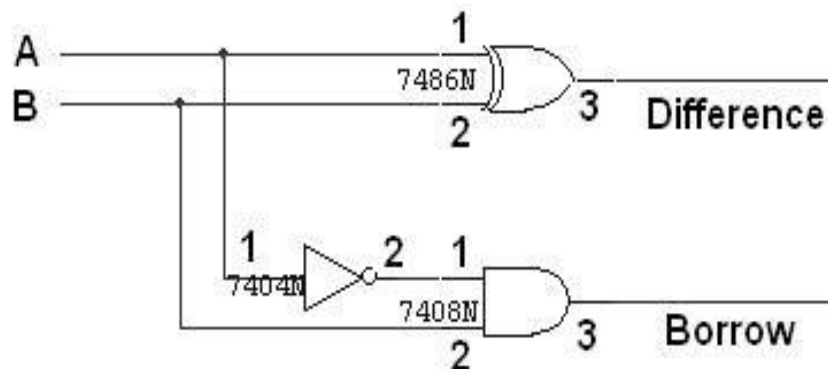

TRUTH TABLE


A	B	BORROW	DIFFERENCE
0	0	0	0
0	1	1	1
1	0	0	1
1	1	0	0

$$0 - 0 = 0$$

$$0 - 1 = 1, \text{ borrow } 1$$

$$1 - 0 = 1$$


$$1 - 1 = 0$$

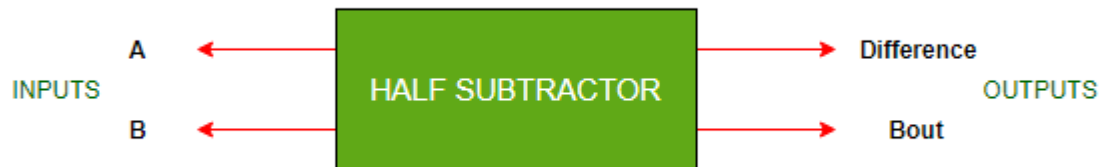


$$\text{DIFFERENCE} = A'B + AB'$$

$$\text{BORROW} = A'B$$

LOGIC DIAGRAM FULL SUBTRACTOR

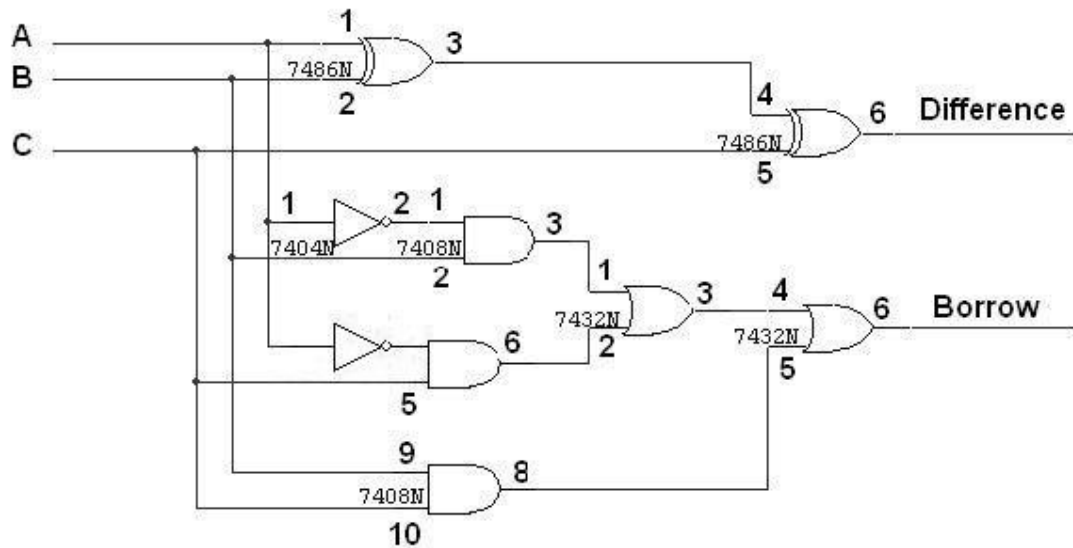


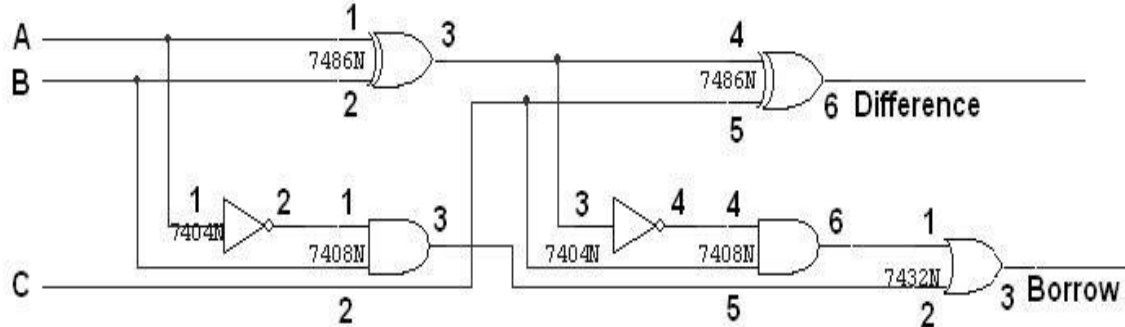FULL SUBTRACTOR USING TWO HALF SUBTRACTOR



TRUTH TABLE

A	B	C	BORROW	DIFFERENCE
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	1	0
1	0	0	0	1
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1

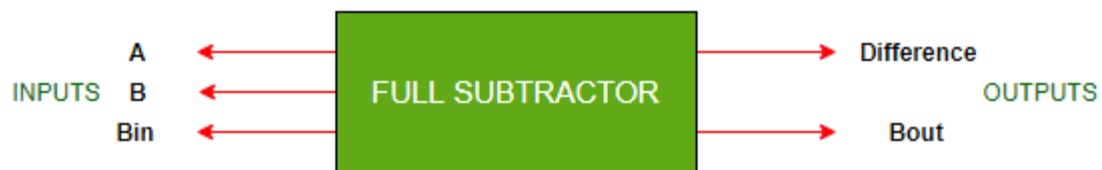


$$\text{BORROW} = A'D + BD + A'B = A'(B+D) + BD$$


PROCEDURE


1. Connections are given as per circuit diagram.
2. Logical inputs are given as per circuit diagram.
3. Observe the output and verify the truth table.


LAB WORK:

HALF ADDER

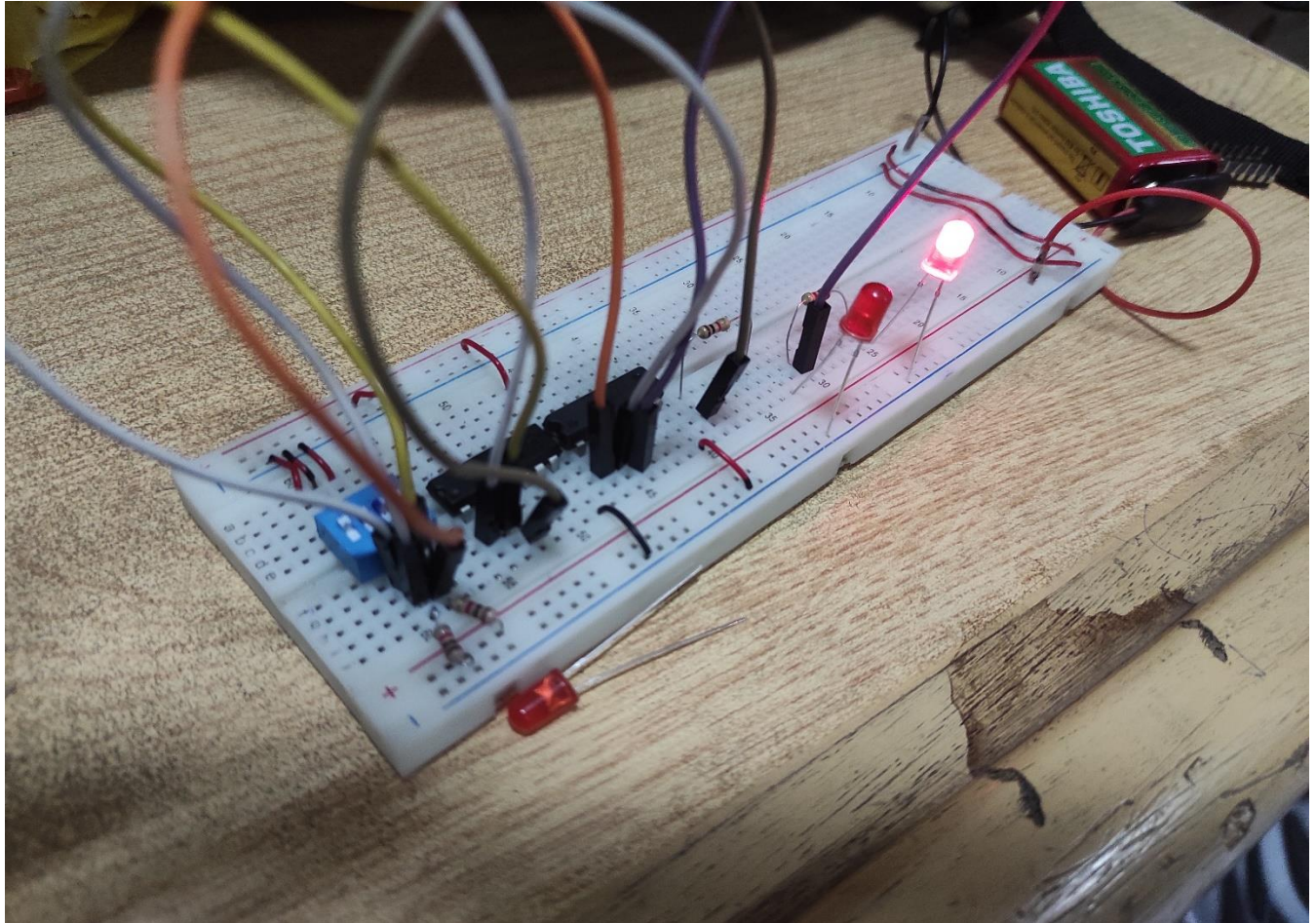


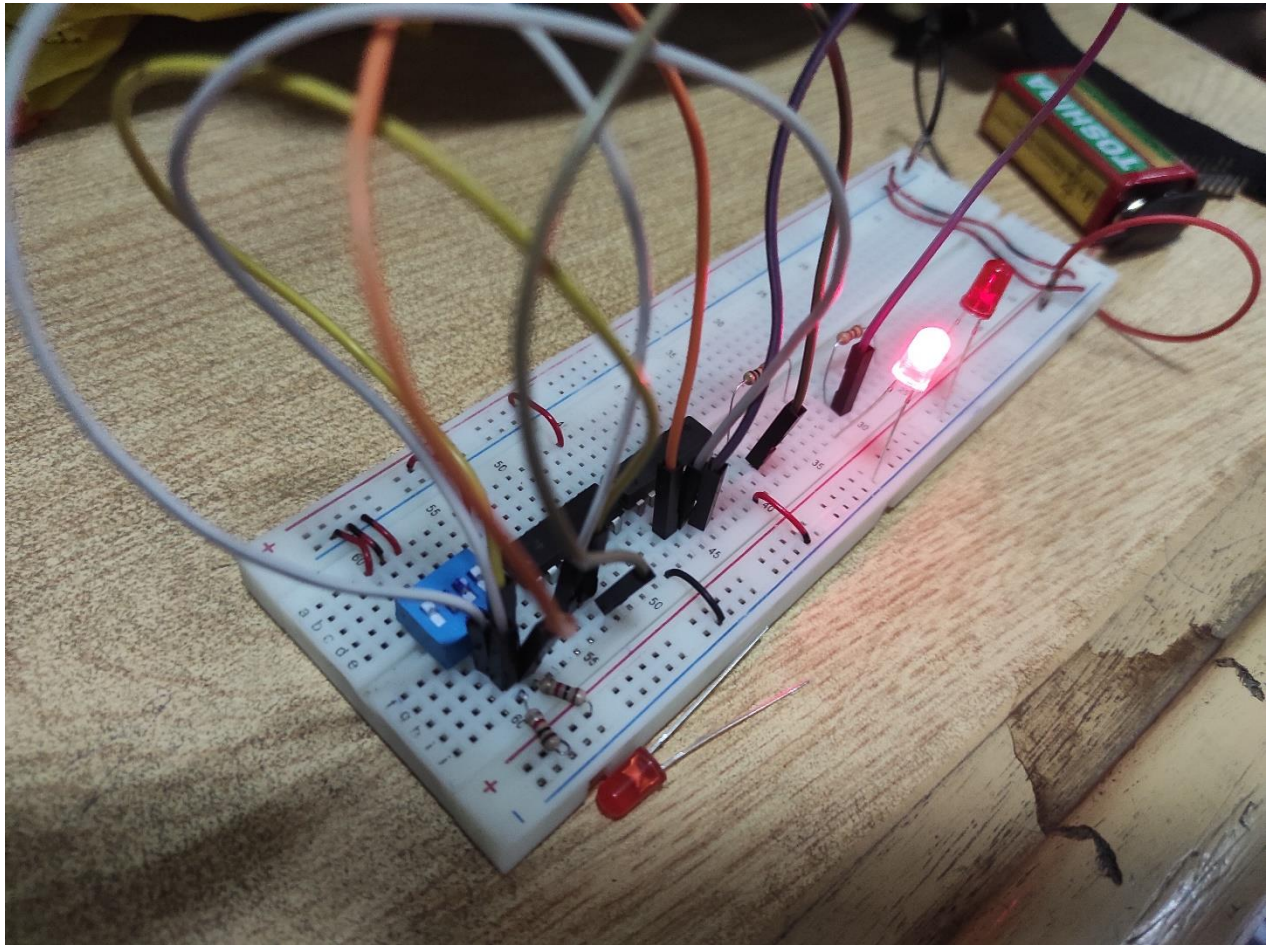


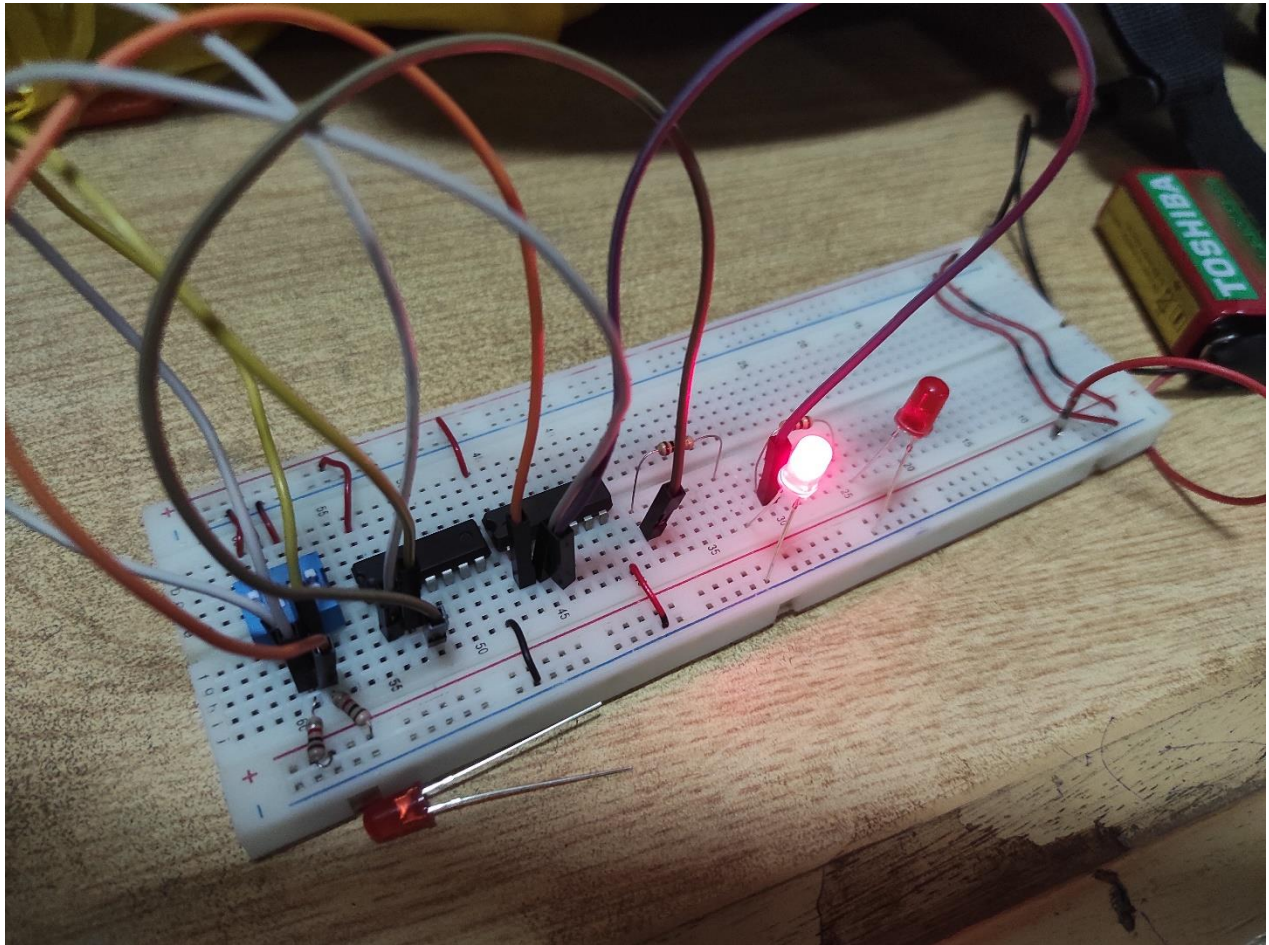

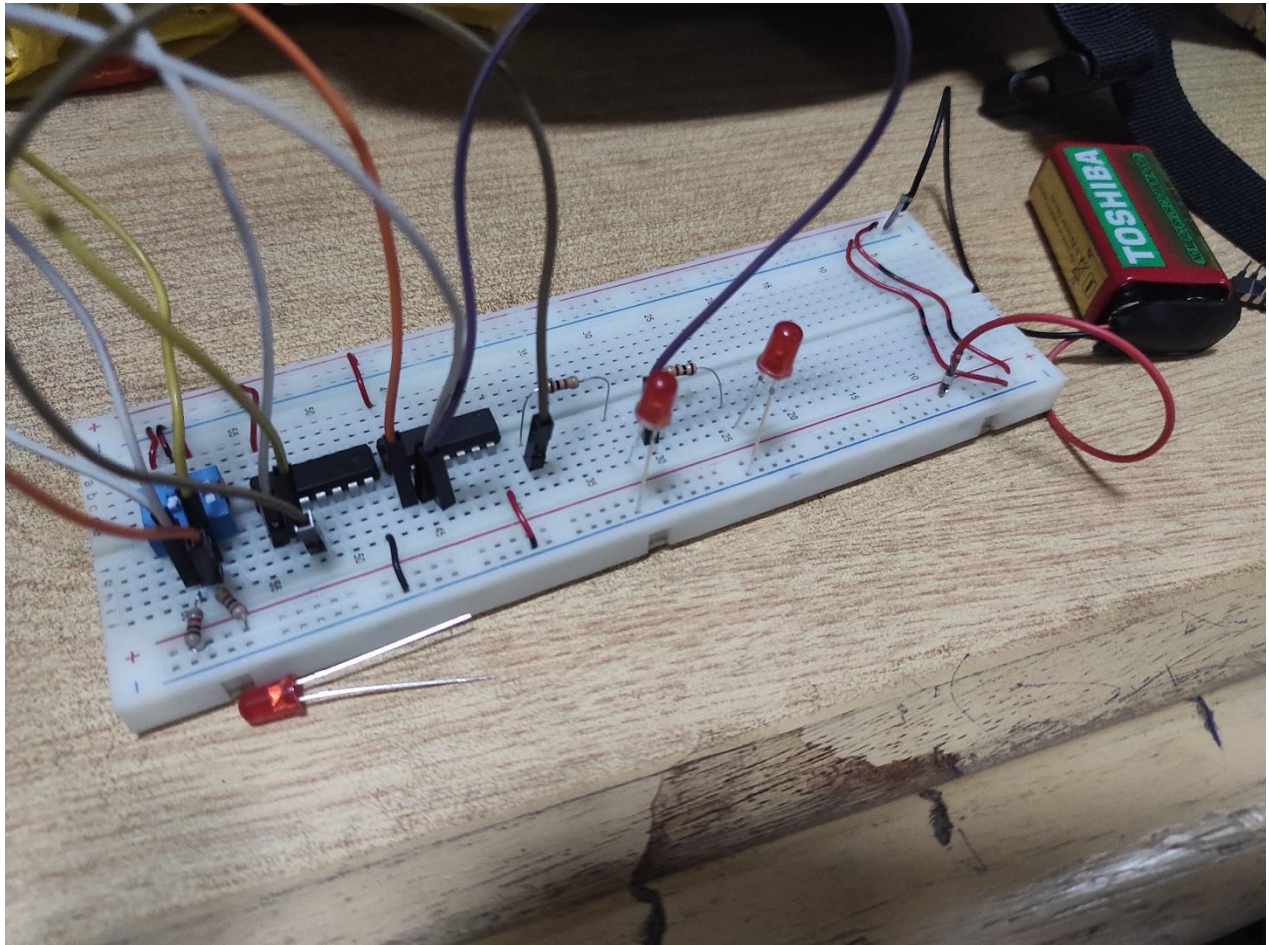



FULL ADDER

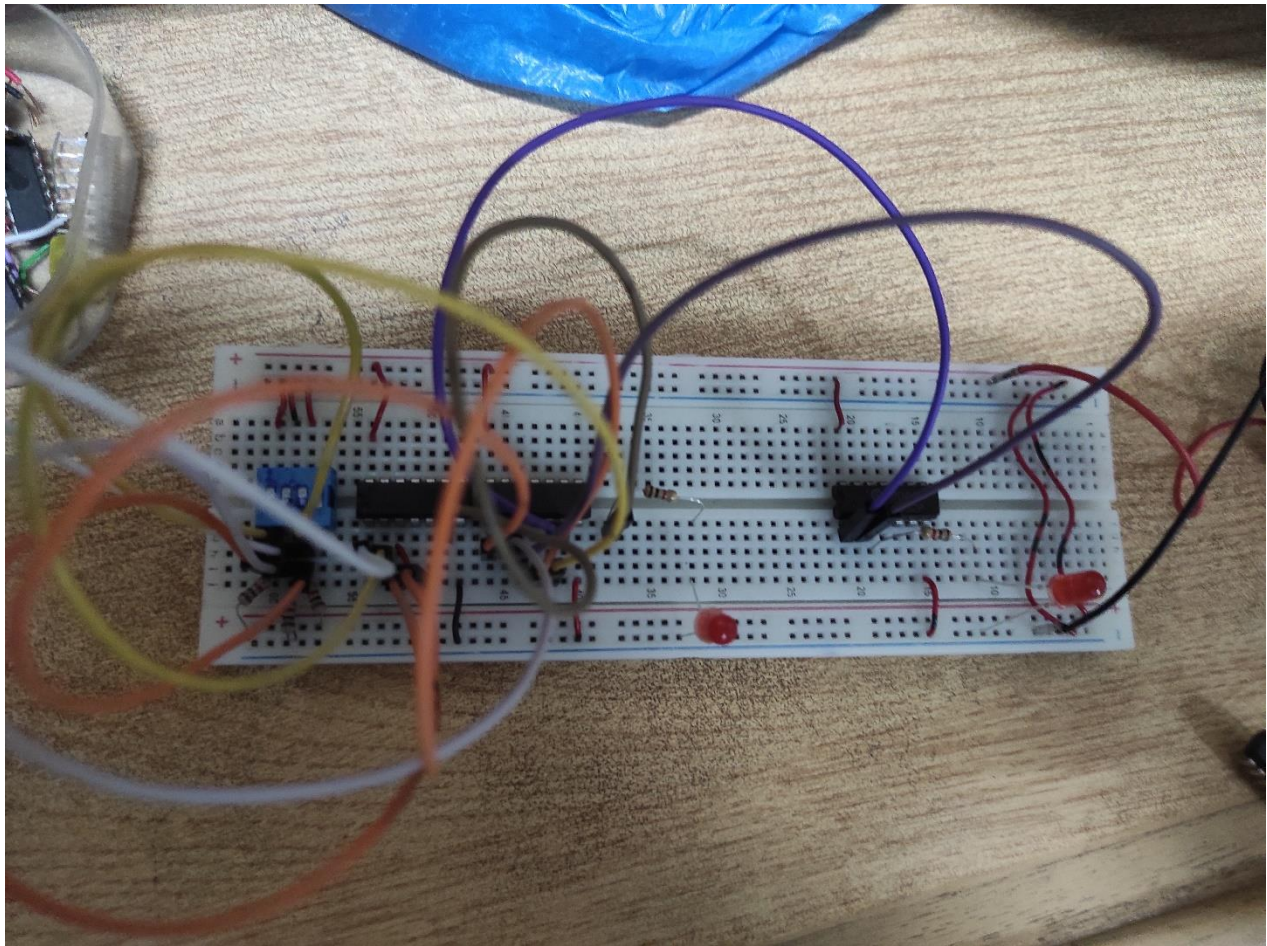


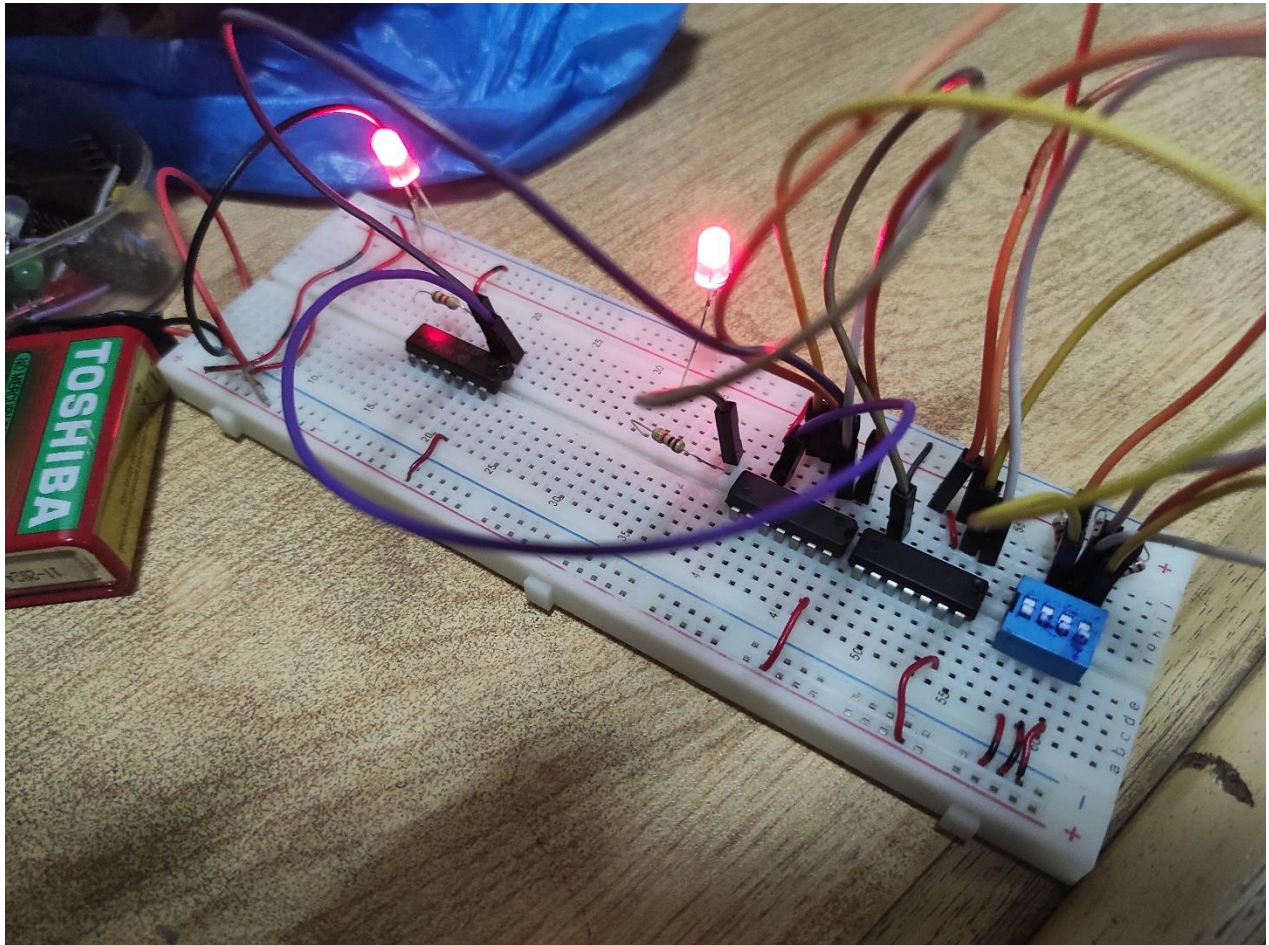


HALF SUBTRACTOR

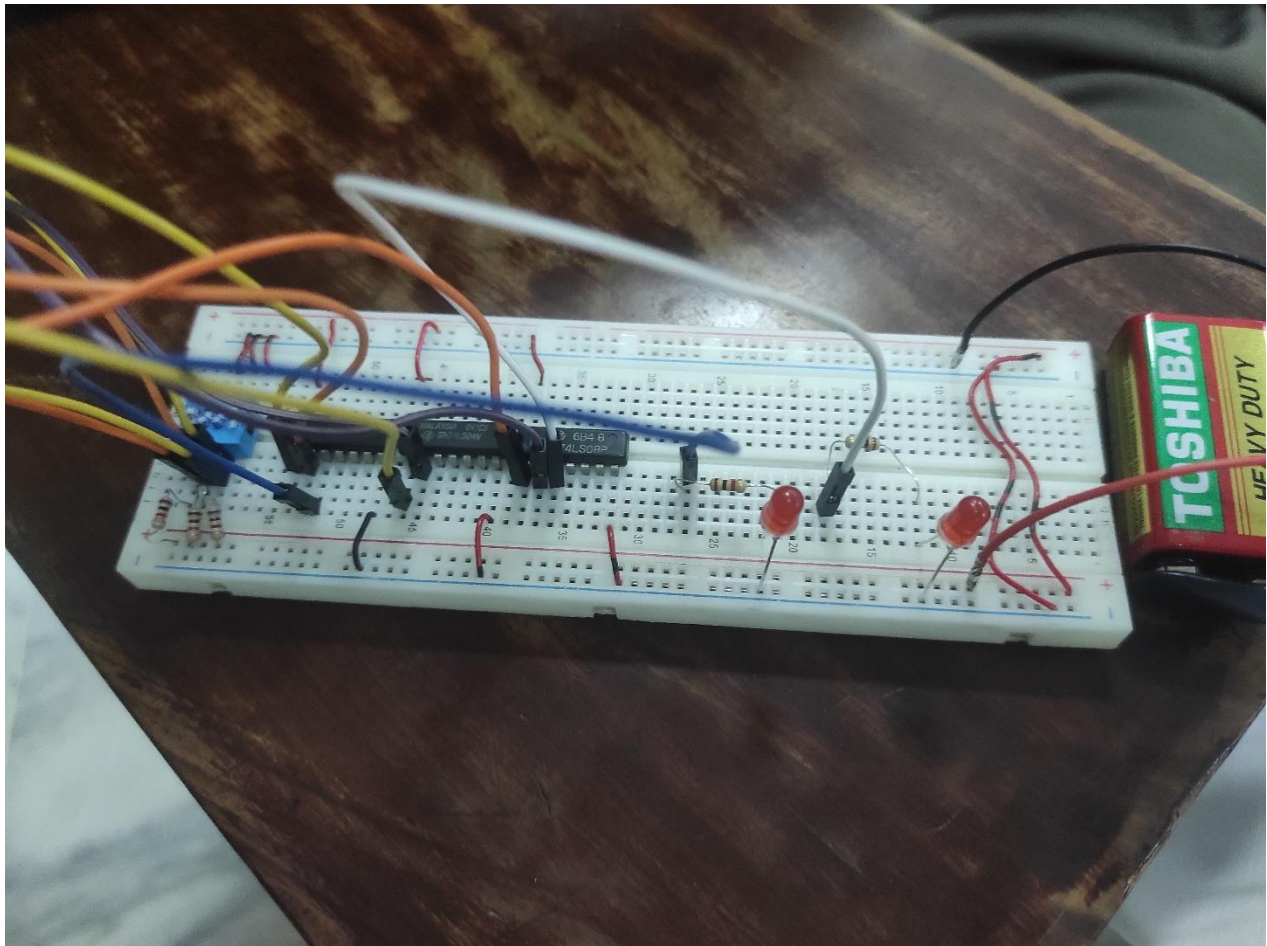

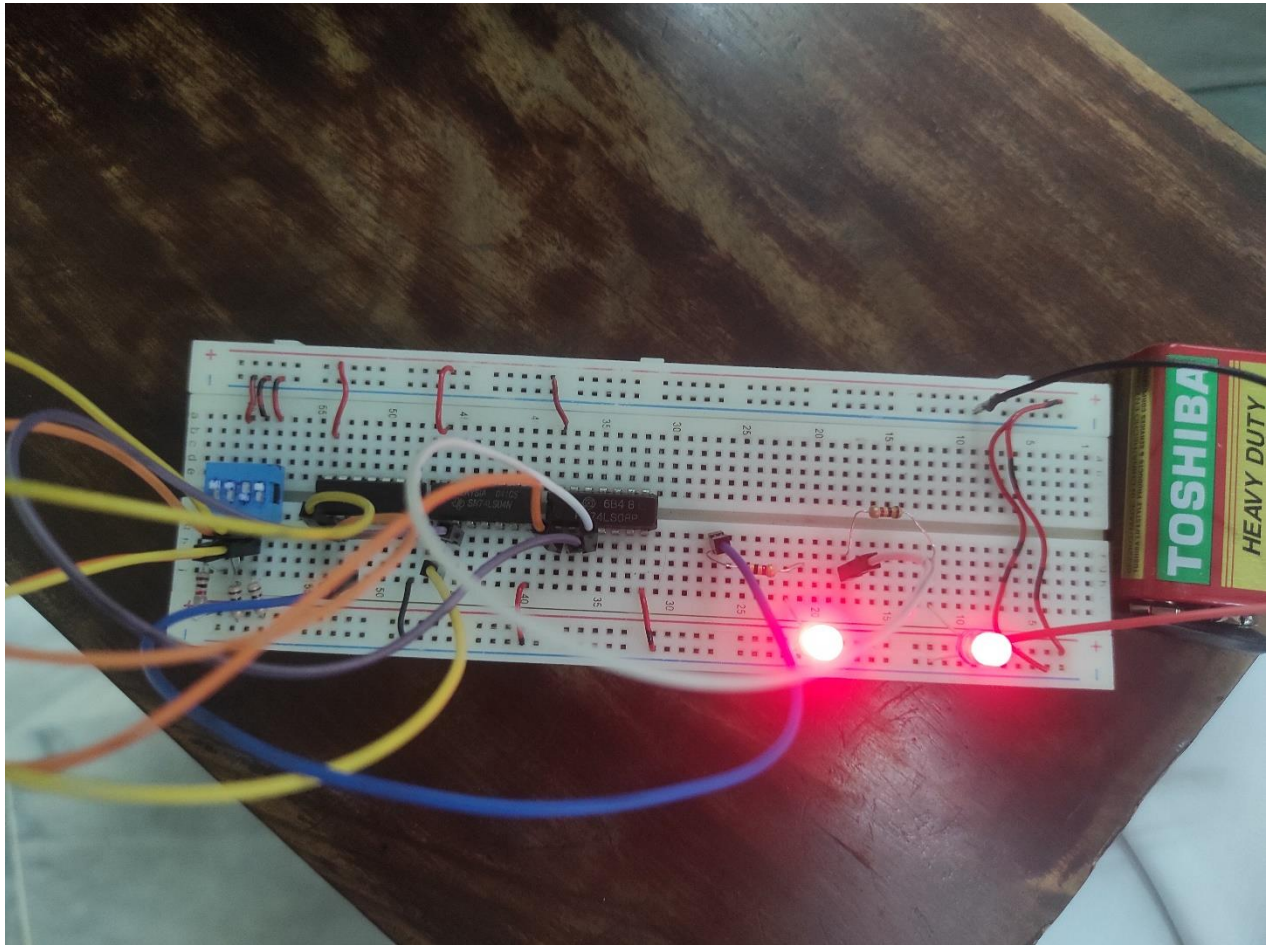

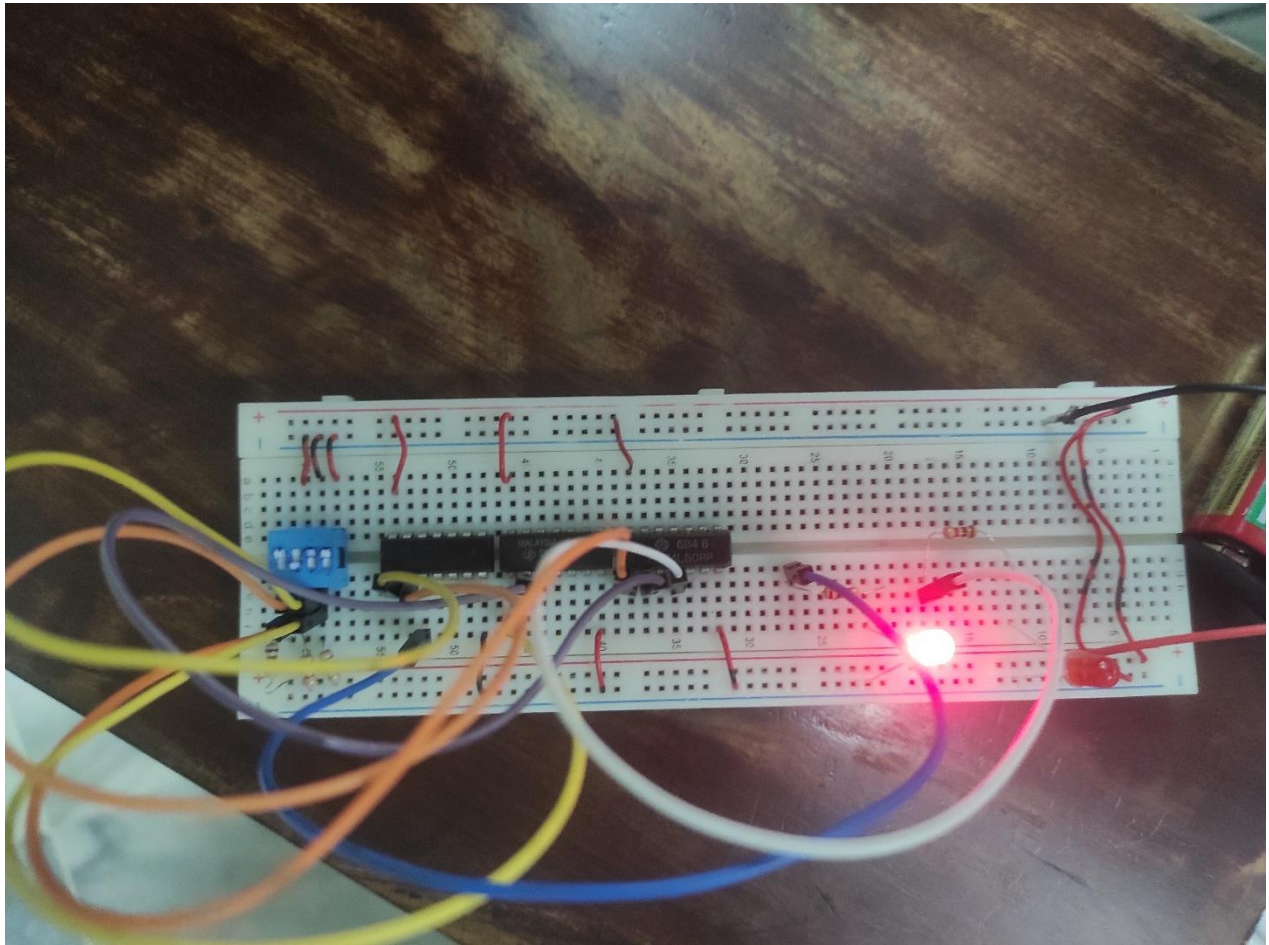

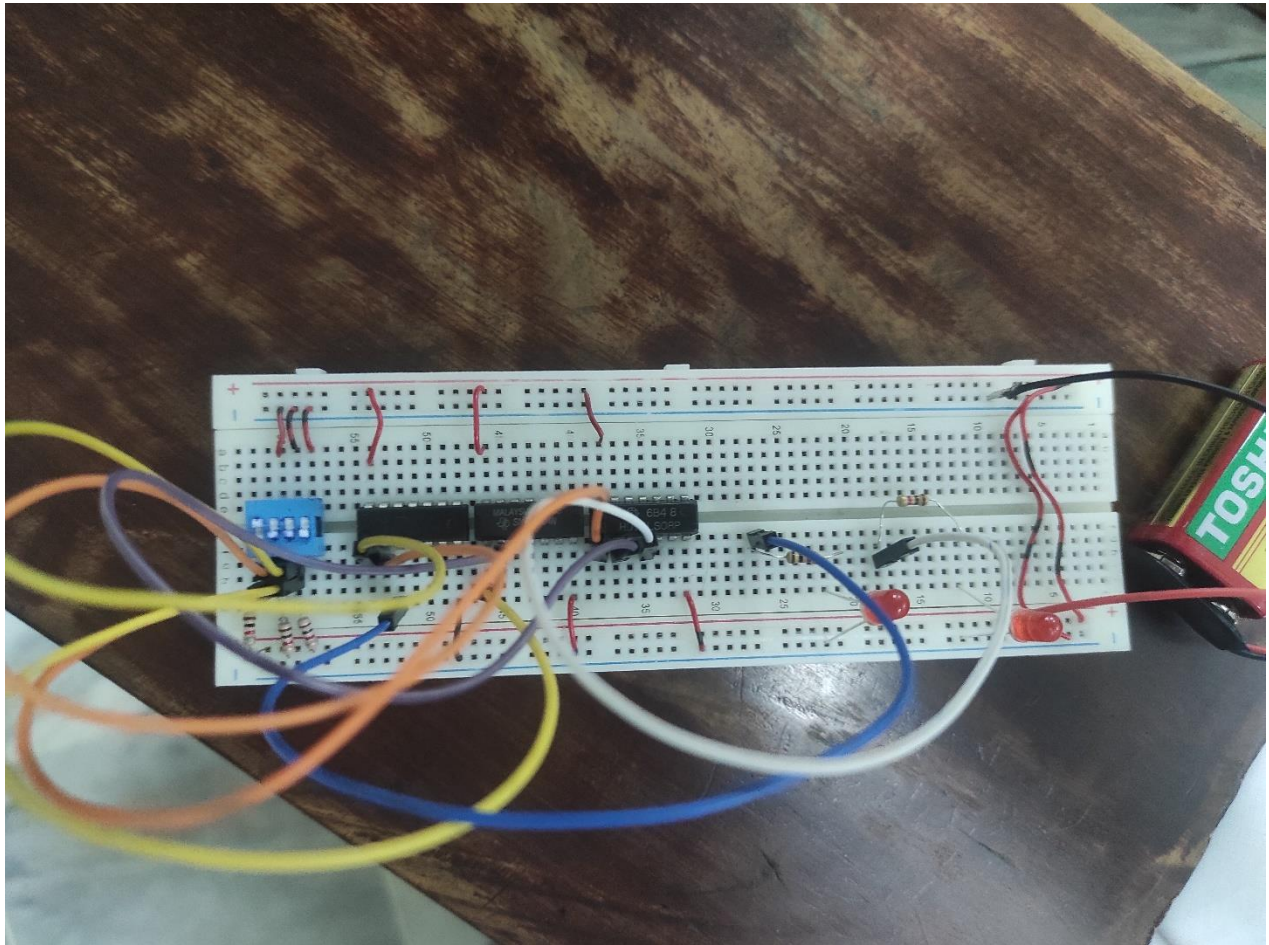

FULL SUBTRACTOR

